



## PHYSICS

# BOOKS - MODERN PUBLISHERS PHYSICS (HINGLISH)

# SEMICONDUCTOR ELECTRONICS METERIALS DEVICES AND SIMPLE CIRCUITS

**Solved Examples** 

1. The number of conduction electrons in a pure semiconductor is  $5 imes10^{18}$  per cubic metre calculte the number of holes in a sample of size 2cm imes1cm imes2mm

**Watch Video Solution** 

**2.** Energy of an electramagnetic radiation of wavelenght 590 nm equals the band gap of a semiconductor calculate the minimum energy required to create an electron hole pair



**3.** A p type semiconductor has acceptor level 30 mev above the valence band what will be the maximum wavelength of light that can create a hole

Watch Video Solution

**4.** Pure Si crystal at 300 k has  $2.5 \times 10^{28}$  atoms  $m^{-3}$  it is doped by 1 ppm concentration of pentavalent element As calculate the new

concentration of electrons and holes take

$$n_i = 1.5 imes 10^{16} m^{-3}$$

#### Watch Video Solution

5. A semiconductor crystal has equal electron and hole concentration of  $9 \times 10^8 m^{-3}$  it is doped by indium so that the hole concentration increases to  $4.5 \times 10^{12} m^{-3}$ calculate the new concentration of free electrons in the doped crystal nad also mention its type



**6.** Mobilities of electrons and holes in a sample of a semiconductor is 25000  $cm^2V^{-1}s^{-1}$  and 200  $cm^2$  Vs respectively if the electron and hole concentration are  $9 \times 10^{13}$  per  $cm^3$  and  $4 \times 10^{12}$  per  $cm^3$  respectively calculate the conductivity of the sample

#### Watch Video Solution

7. An n type semiconductor of conductivity 6  $\Omega^{-1}cm^{-1}$  is produced when donor atoms are added to an intrinsic germanisum crystal ignoring the contributio of holes to conductivity and taking mobility of electron in n type Ge equal to 3500  $cm^2$  /Vs determine the number density of donor atoms used for doping





**9.** The V-I characteristic of a silicon diode is as show in the following calulate the resistance

of the diode at (i)  $I_D=15\,$  mA and (ii)

$$V_D = 10$$
 V

### View Text Solution

**10.** The following table provides the set of values of V and I abtained for a given diode

Assuming the characteristics to be nearly linear and calculate the forwared and reverse bias resistance of the given diode

**View Text Solution** 

**11.** The V-I characteristics of a germainium dioide is shown in the below calculate the diode resistance in forward bias at V= +1.75 V and (b) reverse at V=-1 V





**12.** A p-n junction diode is designed to withstand current without damage up to 5 Ma across the combination. What is the maximum

voltage of the battery that can forward bias the diode safely given that the diode has a constant potential drop of 0.5 V when forward biased



13. Assuming that the silicon diode having resistance of  $20\Omega$ , the current through the

diode is (knee voltage 0.7 V)





Watch Video Solution

**14.** A 2V battery is connected across the points A and B as shown in the figure given below. Assuming that the resistance of each diode is zero in forward bias and infinity in reverse baise, the current supplied by the

connected to A is



**15.** Calculate the currents through the resistance of the circuits shown in the following figure consider the diodes to be







16. In the circuite shown below calculate the curretn flowing through the cirucit and potential differnce across the diode take the drift current for the diode equal to 20  $\mu A$ 







**18.** The following figure shows the circuit for using zener diode of 10 V as a voltage regulator the zener diode is connected in series with a resistor r acorss a 50 V supply claculate the minimum value of r if the the maximum zener current is 25 mA





19. A crystal diode of internal resistance 100  $\omega$ is used as a half wave rectifier as shown in the figure with AC input of V=50 sin wt and load resistance  $R_L = 1k\omega$  calculate

(i) the maximum output current

(ii) DC output current (iii) DC output power







**20.** In a p n p transistor circuit 80% of the holes reach the collector if the collector current is 9 mA calculate the emitter and base curernts



**21.** The ac current gain of a transistor is 120. What is the change in the collector current in

the transistor whose base current changes by

 $100 \mu A$ ?



22. In a common emitter transistor circuit the valtage drop across the collector is 1 V and curent gain is 70 if the collector resistor is 3 k  $\omega$  calculate the base current

Watch Video Solution

**23.** A common emitter amplifier has a current gain of 59 if the emitter current is 5.0 mA find its base current and collector current



24. Current gain of a transistor is 50 if the collector resistance is 5 k  $\omega$  and input

resistance is 1 k  $\omega$  calculate the voltage gain



25. In a common emitter amplifier change in base current by 10  $\mu A$  and collector current by 1mA if the input resistance of the transistor is 1  $k\omega$  and load resistacne of  $6k\omega$  is used in the circuit calculate (i) the current gain

(ii) the voltage gain

Watch Video Solution

**26.** Output characteristics of an n-p-n transistor in CE configuration is shown in the

#### Fig. Determine



(i) dynamic output resistance (ii) dc current gain and (iii) ac current gain at an opererating point  $V_{CE}=10V$ , when  $I_B=30\mu A$ .

#### Watch Video Solution

**27.** The current gain for a common emtiter amplifier is 50 the collector resistance of the CE amplifier circuit is 2  $k\omega$  and input resistance is 500  $\omega$  if the input voltage is 0.02 V calculate the output voltage Also calculate the power gain of the circuit

Watch Video Solution

**28.** When base current in a silicon transistor is changed by 12  $\mu A$  the input resistance of the

transistor is 650  $\omega$  when this transistor is

uded as a CE amplifier with load resistance of

2 k  $\omega$  calculate

- (i) the current gain
- (ii) transconductance
- (iiii) voltage gain of the amplifer



**29.** An n p-n transistor is uded as a CE amplifier as given below if the current gain is 30 and internal resisitacne of the transistor is 100  $\omega$ 

calculate

(i) collector emitter voltage

(ii) base current

(iii) voltage gain

(iv) power gain





**30.** In the transistor cirucuit the base current  $I_B=5\mu A$  and the collector current  $I_C=5$  mA the dc voltage of the collector circuit

#### $V_{\mathbb{C}}~=6V$



(i) can this circuit be used as an amplifier

(ii) If  $R_C$  is reduced to 500  $\omega$  can the circuit be

then used as an amplifier

View Text Solution

**31.** An amplifier circuit is below having an input resistance  $R_i=25k\omega$  it is connected to an external voltage vs through a eries resistance  $R_S=50\omega$  the no load voltage gain of the

transistor is 150 find the apparent gain of the

#### amplifier





#### **32.** Write the truth table for the combinatio of

#### the gates shown name the gates used





33. Circuit symbol of logic gate and two input wave fronts 'A' and 'B' are in given below(i) Name the gate used and write its truth table

(ii) Draw the output wave form



View Text Solution

**34.** Identify the logic gates  $G_1$  and  $G_2$  marked

in the



write down the output Y when A=1 ,B =1 and

A=1 and B=0

View Text Solution

**35.** Write the truth table for a NAND gate as given in Fig.9. Hence identify the exact logic operation carried out by this circuit.



Watch Video Solution

**36.** For the given combinatin of gates find the values of ouputs  $Y_1$  and  $Y_2$  in the table given below inentify the gates  $G_1$  and  $G_2$ 





**37.** Write the truth table for circuit given in Fig.below consisting of NOR gates and identify the logic operation (OR, AND and NOT) which

this circuit is performing.



### Watch Video Solution

## 38. Write the output Y for the final circuit

when

(i) A=1 and B=1

(ii) A=0 and B=0



**39.** A student has to use an appropriate number of (i) NAND gates (only) to get the output  $y_1$  (ii) NOR gates (only) to get the output  $y_2$  from two given input A and B as shown in the Fig.



Identify the 'equivalent gate' needed in each case. Show how one can connect an appropriate number of (i) NAND (ii) NOR gates respectively in the two cases to gat the equivalent gates.

Watch Video Solution

**40.** Write the truth table for the following

circuit



1. A pure semiconductor of volume  $3.5 imes 10^{-7} m^3$  contains  $5 imes 10^{20}$  conduction electrons per  $m^3$  determine the number of holes present in it

Watch Video Solution

**2.** The mean free path of conduction electron in a metallic block is  $5 imes10^{-6}$  m the block is

placed in an electric field of  $5 imes 10^{+7} vm^{-1}$  calculate the energy of the conduction electron in the block

Watch Video Solution

3. Suppose a pure Si-crystal has  $5 imes 10^{28} \mathrm{atoms} m^{-3}$ . It is doped by 1 ppm concentration of pentavalent As. Calculate the number of electrons and holes. Give that  $n_i = 1.5 imes 10^{16} m^{-3}$ .

4. In pure silicon semiconductor having same electron and hole concentration of  $1.5 \times 10^{16}$ the hole density is increased to 1.5 times on doping calculate the electron density in silicon after doping



5. A semiconductor has equal electron and hole concentration of  $6 imes10^8m^{-3}$  on doping with certain impurity electron concentration



6. The separation between conduction band of

electromagnetic radiation required to

generate an electron hole pair in ti

View Text Solution

**7.** The fobbidden gap in an ntype semiconductor is 4 me v so that the electrons are just able to enter the coduction band



8. A type semiconductor sample has electron and hole concentration of  $1.6 \times 10^{19}$  the electron and hole mobility in the sample is  $1.2m^2v^{-1}s^{-1}$  and 0.001  $m^2v^{-1}s^{-1}$
respectively calculate the value of resistivity of

the sample



**9.** The value of forward current in ap-n junction at 0.1 V is  $1.04 \times 10^{-2}$  A calculate the reverse saturation current of the diode at 300 k kuse bottzmann's k = $1.4 \times 10^{-23} j K^{-1}$  and exp (3.80)=44.7011

10. The values of v and I for silicon diode is

given as follows

	V	I
Forward bias	1.0 V 0.80 V	10 mA 6 mA
Reverse bias	-2 V -4 V	3 mA 2 mA

Using the data calculate the forward and

reverse bias resistance of silicon diode

Watch Video Solution

**11.** Voltage drop across a p-n junction in forward bias is 0.5 V a battery of 2V is

connected across the p-n junction such that the maximum current does not exceed 10 mA calculate the value of resistance to be connected across the diode



Watch Video Solution

**12.** A p-n junction diode in forward bias is connected to a battery of 4 V and a resistance of 80  $\omega$  as shown in the ajoining determine the maximum current in the circuit barrier

#### potential of p-n diode is 0.2 V



**13.** Two diodes with internal resistance of 20  $\omega$  each are used in a full wave rectifier determine the mean load current and rms value of load

current if load resistance of 800  $\omega$  given rms

value of secondary voltage is 40 V



14. The rms value of input voltage in a full wave rectifier is 12 V determine the output voltage if a step up a transformer with ratio1:2 is used

15. In a Zener regulated power supply a Zener diode with  $V_Z = 6.0V$  is used for regulation. The load current is to be 4.0 mA and the unregulated input is 10.0 V. What should be the value of series resistor  $R_S$ ? Choose zener current to be 20 mA.



**16.** A 10V of zener diode is connected in series to a resistance across a power supply of 50 V calculate the minimum value of resistance required such that the zener current is 25 mA

Watch Video Solution

**17.** From the output characteristics of common emitter circuit shown in Fig., calculate the value of  $\beta_{ac}$  and  $\beta_{dc}$  of the transistor when







**18.** In a common emitter transistor the potential drop across the collector is found to be 2 v claculate the emitter current if value of

collector resistance is 2  $k\omega$  the dc gain of

transistor is 40



**19.** In a common base transistor the value of load resistance in output and input circuit is 500  $k\omega$  and 300  $\omega$  respectively calculate the voltage gain and power gain if value of current gain is 0.90



**20.** In a semiconductor transistor there is change in collector current of 8.2 mA with change of 8.29 mA in emitter current calculate the change in base current that produces same change in collector current

Watch Video Solution

21. In common emitter transistor as shown in Fig., the  $V_{BB}$  supply can be varied from 0 V to 5.0V. The Si. Transistor has  $\beta_{ac} = 250$  and  $R_B = 100k\Omega, R_c = 1k\Omega, V_{CC} = 5.0V.$ 

Assume that when the transistor is saturated,  $V_{CE} = 0V$  and  $V_{BE} = 0.8V$ . Calculate the minimum base current, for which the transistor will reach saturation. Hence, determine  $V_i$  when the transistor is 'switched on' find ranges of  $V_i$  for which the transistor is switched off and switched on.



**22.** For a CE transistor amplifier the audio signal voltage across the collector resistance of 2.0  $k\omega$  is 2.0 V suppose the current amplification factor of the transistor is 100 what should be the value of  $R_B$  in series with  $V_{BB}$  10 times the signal current also calculate the DC drop across the collector resistance

#### 23. Which gate is represented by the given

#### truth table





**24.** You are given a circuit below write its truth table hence identify the logic operation carried out by the circuit draw the logic

symbol of the gate it corresponds to



Watch Video Solution

**25.** Identify the logic gates marked P and Q in the circuit Fig. Write the truth table for this combination.







### **Concepual Questions**

1. C, Si and Ge have same lattice structure. Why

is C insulator,

while Si and Ge intrinsic semiconductors ?



## 2. What type of inter atomic bonding is there

in semiconductors



**3.** Why doping is done in semiconductor?



4. Can we take one slab of p - type semiconductor and physically
join it to another n - type semiconductor to get p - n junction?



5. How does the width of the depletion layer of

a p-n junction diode change with decrease in

reverse bias?



6. Intrinsic and extrinsic semiconductors .



7. p-type and n-type semiconductors .



# 8. A p - type semiconductor crystal is electrically neutral although it has larger number of holes explain

**Watch Video Solution** 

**9.** In a semiconductor energy gap between the impurites level and conduction band is 1 me V is it an n type or p type of semiconductor





10. Out of electron and hole, which one has

higher mobility and Why?



11. How does the forbidden energy gap of an

intrinsic semiconductor vary with the increase

in temperature

**12.** An intrinsic semiconductor is doped with boron how will the energy gap change in semiconductor



**13.** An intrinsic semiconductor is doped with arsenic how will the energy gap change in

semiconductor



**14.** What will happen to the conductivity of a semiconductor on passing large currents through it

**O** Watch Video Solution

**15.** Graphically represent the variatin of resistivity of carbon with temperture

16. Why si and gaas are preferred material for

solar cells

Watch Video Solution

**17.** The resistance of p-n junction is low when forward biased and is high when reverse biased. Explain.

**18.** A p n junction diode is connected to a battery of 2 v and a resistance of 8 ohm as shown in figure calculate the current passing through the resistor

**Watch Video Solution** 

**19.** A p -n junctin diode is connected to a battery of 2 V and a resistance as shownin the adjoining calculate the curernt passing





**20.** A half wave rectifier provides DC output power of 30 W when 100 W AC power is supplied to it what will be the rectification efficiency and power efficiency





**23.** In a transistor base is made thin and doped with little impurity atoms. Why?

Watch Video Solution

24. How will the current in the transistor

change with the increase in temperature

25. Explain, why the input resistance of a transistor is low and output resistance is high. Watch Video Solution 26. Transistor also works bidirectinaly comment Watch Video Solution

**27.** In a transistor both emitter base jucntion and colector base junction are reverse biased how will the concentration of charge carrier across the each junction change



**28.** If the base region of a transistor is made large, as compared to a usual transistor, how does it affect (i) the collector current and (ii) current gain of this transistor.



**29.** In the given circuit diagram, a voltmeter 'V' is connected across a lamp 'L'. How would (i) the brightness of the lamp and (ii) voltmeter reading 'V' be affected, if the value of resistance 'R' is decreased ? Justify your answer.



30. How are analogue and digital signals different

 Watch Video Solution

31. Discuss how a NOT gate is realised using

NAND gates.

32. Realise the formation of AND gate using

NAND gate

Watch Video Solution

33. Realise the formation of OR gate from

NAND gate





# 35. NAND gate is also known as digital

building block explain

**36.** Arrange two NAND gates and one OR gate such that the combination obtained acts as the NAND gate only

Watch Video Solution

**37.** The following Fig. shows the input waveforms (A,B) and the output waveform (y) of a gate. Identify the gate and write its truth

table.



1. The number of electron hole pairs in a semiconductor is proportional to where for germainium  $\triangle E = 0.65$  eV and the temperature increases form 280 K to 300 K find the percentage increase in the number of charge carriers


**2.** An n-p-n transistor is used as a simple voltage amplifier in common emitter mode. when a signal of 30mV is added to base emitter voltage results a change in base current by 40 micro ampere and collector current changes by 2 mA given that the load resistance is 5  $k\omega$  calculate

(i) current gain

(ii) input resistance

(iii) transconductance

(iv) voltage gain



**3.** A potential barrier of 0.2 V exists across an unbiased p-n junction

(i) Calculate the width of the depletion region if an electric field of  $10^6 Vm^{-1}$  exists in it (ii) With what minimum kinetic energy a hole should diffuse from the p side to the n side if the junction is

(a) unbiased

(b) forward biased at 0.1 V

(c) reverse biased at 0.1 V



**4.** A p-n junction when forward biased at 100 mV has a current of 50  $\mu A$  and when reverse biased it has a constant current of 20  $\mu A$  flowing through it Calculate the magnitude of diffusion current

when the diode is

(i) unbiased

(ii) forward biased at 100 mV

(iii) reverse biased at 100 mV



5. Using AND ,Not and OR gates desigin a local

circuit to evalute ABC+ABC+BAC



6. A sample of pure silicon is doped with a trivalent impurity whose each atom creates a hole the concentration holes in pure silicon is  $7 \times 10^{15}$  holes per cubic metre and density of silicon is  $5 \times 10^{23}$  a pure silicon sample by a

factor of 120 calculate approximately the

proportion in which the impurity is added



7. An AC voltage with peak value 20 V is connected in series a diode and load resistance of 500  $\omega$  exists across the diode calculate the peak current through the diode and peak voltage across the load resistance what will be the answer if the diode is ideal



**8.** A zener diode has a breakdown voltage of 10 V and is used in a voltage regulator circuit as shown in the given figure what will be current





9. The relation of voltage with current in a

diode is expressed as below

$$V = \frac{1000In(I+1)}{T}$$

where v is the applied voltage in volts

T is the temperature in degree kelvin and I is the current in milli amperes while measuring a

current of 10 mA at T=300 k a student makes an error of  $\pm\,$  0.01 V calculate the error in the value of current in mA

Watch Video Solution

**10.** (i) the number of conduction electrons in a sample of pure semiconductor is  $7 \times 10^{20}$  per cubic metre calculate the number of holes in a sample of size  $2cm \times 2cm \times 2cm$ (ii) an electron in the conduction band combines with a hole in the valence band of the semiconductor and excess energy is released in the of the semiconductor is 2.1 eV find the maximum wavelength that can be emitte in this process

**Watch Video Solution** 

### Ncert File Solved Text Book Exercises

1. In an n type silicon which of the following

statement is true

(a) electrons are majortiy carriers and trivalent

atoms are the dopants

(b) electrons are minority carriers and pentavalent atoms are the dopants
(c) hoes are minority carriers and pentavalent atoms are the dopants
(d) holes are majority carriers and trivalen atoms are the dopant

**2.** Which of the statements given in above example is true for p - type semiconductors ?



**3.** Carbon silicon and germanium have four valence electrons each these are characterised by valence and conduction bands separated by energy band gap respectively equal to which of the following statement is true (a)  $\left(E_g\right)_{S_i} < \left(E_g\right)_{G_e} < \left(E_g\right)_c$ (b)  $\left(E_g
ight)_{c} < \left(E_g
ight)_{Ge < \left(E_g
ight)_{Gi}}$ (c) $\left(E_{g}
ight)_{c}>\left(E_{g}
ight)_{Si}>\left(E_{g}
ight)_{Ge}$  $(d) \left( E_{g} \right)_{c} = \left( E_{g} \right)_{ci} = \left( E_{g} \right)_{Ce}$ 

4. In an unblased p-n junction, holes diffuse

from the p - region to n- region because



**5.** When a forward bias is applied to a p -n junction. It

6. For transistor action which of the following statement are correct (a) base emitter and collector regions should have smilar size and doping concentrations (b) the base region must be very thin and lightly doped (c) the emitter junction is forward biased and collector junctions is reverse biased (d)both the emitter junction as well as the collector junction are forward biased

7. For transistor amplifier the voltage gain
(a) remains constant for all frequencies
(b) is high at high and low frequencies
(c) is low at high and low frequencies and
constant in the middle frequency range
(d) none of these

Watch Video Solution

**8.** In half - wave rectification, what is the output frequency, if the

input frequency is 50 Hz ? What is the output

frequency of a full - wave rectifier

for the same input frequency?

Watch Video Solution

**9.** For a CE -transistor amplifier the audio signal voltage across the collector resistance of 2 k $\Omega$ is 2V. Given the current amplification factor of the transistor is 100 find the input signal voltage and base current if the base resistance is 1 k  $\Omega$ .



**10.** Two amplifiers are connected one after the other in series (cascaded). The first amplifier has a voltage gain of 10 and the second has a voltage gain of 20 . If the input signal is 0.01 V , calcualte the output AC signal .

Watch Video Solution

**11.** A p-n photodiode is fabricated from a semiconductor with band gap of 2.8 eV can it

# detect a wavelength of 6000 nm



12. The number of silicon atoms per  $m^3 is5 \times 10^{28}$ . This is doped simultaneously with  $5 \times 10^{22}$  atoms per  $m^3$  of Arsenic and  $5 \times 10^{20} perm^3$  atoms of indium. Calculate the number of electrons and holes. Given that  $n_i = 1.5 \times 10^{16} m^{-3}$ . Is the material n-type or p-type?

**13.** In an intrinsic semiconductor, the energy gap  $E_q$  of an intrinsic semiconductor is 1.2 eV. Its hole mobility is very much smaller than electron mobility and is independent of temperature. What is the ratio between conductivity at 600K and at 300K? Assume that the temperature dependence of intrinsic concentraction  $n_i$  is expressed as,

 $n_i=n_oe^{-E_g'\,/\,k_B}T$ , where  $n_o$  is constant and  $E_g'$  is an energy equal to  $E_g\,/\,2$ , $k_B=8.62 imes10^{-6}eVK^{-1}.$ 

**14.** In a p-n junction diode, the currect I can expressed as  $I = I_0 \exp \Bigl( rac{eV}{2k_BT} - 1 \Bigr)$  where  $I_0$  is called the reverse saturation current, V is the voltage across the diode and is positive for forward bias and negative for reverse bias, and I is the current through the diode,  $K_B$  is the Boltzmann constant  $(8.6 imes 10^{-5} eV/K)$ and T is the absolute temperature. If for a given diode  $I_o = 5 imes 10^{-12} A$  and T = 300 K,

Watch Video Solution

then

(a) What will be the forward current at a formward voltage of 0.6V? (b) What will be the increase in the current if the voltage across the diode is increased to 0.7V?

(c) What is the dynamic resistance?

(d) What will be current if reverse bias voltage

changes from 1V to 2V?

**15.** You are given two circuits as given below show that circuit (a) acts as OR gate while the

circuit (b) acts as AND gate



Watch Video Solution

**16.** Write the truth table for a NAND gae connected as given in the following



**17.** Why are elemental dopants for Silicon or Germanium usually chosen from group XIII or

group XV?

18. Sn, C, Si and Ge are all group XIV elements .Yet , Sn is a conductor , C is an insulator whileSi and Ge are semiconductors . Why?



**19.** Can the potential barrier across a p-n junction be measured by simply connecting a

voltmeter across the junction ?



20. Draw the output wave form across the

resistor



Input waveform at A



**21.** The amplifiers X, Y and Z are connected in series. If the voltage gains of X, Y and Z are 10, 20 and 30, respectively and the input signal is 1mV peak value, then what is the output

signal voltage (peak value)

(i) if dc supply voltage is 10V ?

(ii) if dc supply voltage is 5V?

Watch Video Solution

22. In a CE transistor amplifier, there is a current and voltage gain associated with the circuit. In other words there is a power gain. Considering power a measure of energy, does the circuit violate conservation of energy ?



23. (i) Name the type of a diode whose characteristics are shown in figure (a) and (b)
(ii) What does the point P in fig. (a) represent ?
(iii) What does the point P and Q in fig. (b) represent ?



24. Three photodiodes  $D_1$ ,  $D_2$  and  $D_3$  are made of semiconductors having band gaps of 2.5eV, 2eV and 3 eV, respectively. Which one will be able to detect light of wavelength 6000Å?

Watch Video Solution

**25.** If the resistance  $R_1$  is increased how will the reading of the ammeter and voltmeter

#### change





**26.** Two car garages have a common gate which needs to open automatically when a car enters either of the garages or cars enter both. Devise a circuit that resembles this situation using diodes for the situation .



27. How would you set up a circuit to obtain

NOT gate using a transistor?

**Watch Video Solution** 

28. Explain why elemental semiconductor

cannot be used to make visible LEDs.

#### 29. Write the truth table for the circuit shown

in name the gate that the circuit resembles



**30.** A Zener of power rating 1 W is to be used as a voltage regulator. If Zener has a breakdown of 5V and it has to regulate voltage which fluctuated between 3 V and 7 V, what should be the value of  $R_s$  for safe operation (see figure) ?



# Higer Order Thinking Skills Advanced Level

1. Impurity levels in a doped semiconductor is found to be 35 millielectron volts below the conduction at temperature  $T_1$  when thermal collisions take place approximate amount of energy and reach the conduction band due to collisions then estimate the temperature of the sample



2. In semiconductors, thermal collisions are responsible for taking a valence electorn to the conduction band.Why does the number of conduction electrons not go on increasing with time as thermal collisions continuously take place?

Watch Video Solution

**3.** When a p-type impurity is doped in a semiconductor, a large number of holes are

created. This does not make the semiconductor chared.But when holes diffuse from the p-side to the n-side in a p-n junction,the n-side gets positvely charged.Explain.

**4.** A zener diode of power rating 2 W is to used as a voltage regulator if the diode has a breakdown voltage equal to 10 v and has to gregulate voltage fluctuating between 8V and 12 v calculate the value of R for safe operation



5. If the two ends of a p-n junction are joined by a wire will there be steady current in the circuit if yes then specify its direction

**6.** Calculate the number of states per cubic metre of sodium in 3s band. The density of sodium is  $1013kgm^{-3}$ . How naby of them are empty?

Watch Video Solution

7. A semiconductor material x is made by doping a germanium crystal with indium another semiconductor material y is made by doping a x nad y ar then joined together and
#### connected to a battery



will the jucntion be forward or reverse biased

also draw the V-I characteristics for the circuit



**8.** A student constructed an inexpensive lamp using a diode to allow light contro via a switch

positin as the reversal of be either dim or brigh another switch is provided for ON/OFF mode



Explain the functioning of this cirucit by how it is able to make the lamp glow brighter or dimmer

if we reverse the orientiatio of the diode how

will the lamp behave

**9.** A photodiode is operated in reverse mode under different illumination intensities  $I_1I_2I_3$ and  $I_4$  if  $I_1 < I_2 < I_3 < I_4$  show reverse bias current for different intensities on a current voltage graph take reverse bias voltage to be same



**10.** The lattice structure for both carbon and silicon is same with each of them having 4 bonding electrons c is an insulator wheres Si is semiconductor why

Watch Video Solution

**11.** The ideal diodes  $D_1$  and  $D_2$  are to be connected in the positions shown in the circuit shown below



calculate the current in the circuit

(i) when p side of  $D_1$  is connected to resistance  $R_1$  and p side of  $D_2$  is connected to resistance  $R_2$ 

(ii) when n side of  $D_1$  connected to resistance

 $R_1$  and n side of  $D_2$  is connected to resistance

 $R_2$ 





## 2. What is fermi level and fermi energy?





Watch Video Solution

**4.** Why diamond behaves like an insulator?

Watch Video Solution

**5.** Draw the output signal in a p-n junction diode when a square input signal of 10 v as is

### applied across it





# 6. Distinguish between intrinsic and extrinsic

semiconductors



7. What is doping why it is done



**9.** What is an extrinsic semiconductor? Discuss the working of the various types of extrinsic

semiconductors with help of their energy

band diagram.



10. How will you dope a pure silicon crystal to

obtain a p type and an n type semiconductor

Watch Video Solution

**11.** p-type and n-type semiconductors .

**12.** Give a comparative discussion on majority and minority carriers in n type and type semiconductors

Watch Video Solution

# 13. When a p-n junction diode is forward

biased how will its barrier potential affected

14. What do you mean by reverse biasing of a p-n diode

Watch Video Solution

15. What is the deffect on current when a p-n

diode is (i) forward biased (ii) reverse biased

Watch Video Solution

16. What is knee voltage





**19.** What happens to the width of depletion layer of a p-n junction when it is (i) forward biased, (ii) reverse biased?



## 20. DYNAMIC RESISTANCE OF THE JUNCTION

DIODE

21. What is the value of a ripple factor for a

half wave and a full wave rectifier

Watch Video Solution

22. What is a zener diode how is it biased in

normal operation



23. What is the order of reverse current in a

reverse biased p-n junction



# 24. Name the junction diode whose I-V

### characteristics are shown adjoining







## **26.** Draw a p-n junction with reverse bias



27. Why are photodiodes used preferably in

reverse bias condition?

Watch Video Solution

28. Why germainum is preferred to silicon for

making seimiconductor devices

**29.** Name the semiconductor device that can be used to regulate an irregulation dc power supply. With the help of I-V characteristics of this device, explain its working.

**Watch Video Solution** 

30. Compare the working principal of an LEF

and a photodiode

## **31.** What is dark current



**34.** What is the function of base region of a transistor? Why is this region made thin and lightly doped?

Watch Video Solution

**35.** In a common base transistor what is the phase relationship between input and output voltage

**36.** In a common emitter amplifier , the phase difference between the input signal voltage and output voltage is

Watch Video Solution

# 37. Why a common emitter amplifer is

preferred toa common base amplifier

**38.** In n-p-n transistor, what are the current carriers inside and outside the transistor circuit?



**39.** In n-p-n transistor, what are the current carriers inside and outside the transistor circuit?



40. Derive a relation between current gain of

common emitter amplifier.



**41.** State the relation for the voltage gain in terms of trans-conductance, using transistor as an amplifier.



**42.** What will be the total voltage amplification

factor when three amplifiers having voltage

gain of 3 are connected in series



### 43. Name a semiconductor device which can be

used as a voltage regulator



44. Why transistor can not be used as rectifier?
Watch Video Solution

**45.** The current amplification factor for CB configuration of a transistor is 0.9 find out the current amplification for CE configuration

**46.** In a transistor, doping level in base is increased slightly. How will it affect (i) collector current and (ii)base current?



## 47. Name the operating region of a transistor

for the use of transistor as an amlopifier



48. Why a logic gate is so named



**50.** Why a NOT gate is also known as an inverter



an AND gate

**Watch Video Solution** 

52. State the rule used in the operation of an

OR gate

**53.** Give the logic symbol of AND gate.





58. How a NOR gate is formed

Watch Video Solution

**59.** Name the optoelectronic device that convert electrical energy in to light

60. How many NAND gates are required to realise (i) OR gates and (ii) AND gate.

61. ICs can be grouped in two categroes what

are they



**Revision Exercises Additoinal Question** 

- 1. Zener diode is used for
  - A. amplification
  - B. dectification
  - C. stabilisation
  - D. all of above

#### **Answer:**



**2.** A semiconductor is cooled form  $T_1K$  to

 $T_2K$ . Its resistance

A. will increase

B. will decrease

C. will not change

D. will first decrease then increase

#### Answer:

3. n type semicondluctor is obtained by adding

impurity to pure semiconductor

A. Trivalent

B. Tetravalent

C. pentavalent

D. all of these

#### Answer:
4. Which of the following symbols represents a

# universal gate







#### **Answer:**

5. What type of semiconductor is obtained by

doping indium with silicon



**6.** A semiconductor is doped with a donor impurity

A. p type

B. n tyhpe

C. n-p-n type

D. p-n-p type





# 7. For a transistor if $\beta$ =100thenalpha` will be

A. 0.99

B. 1.01

C. 100

D. 0.01





# 8. The combination Of NAND gates shown in

## the figure



A. AND gate

B. OR gate

C. NOT gate

D. none of these

#### Answer:



# **9.** Which of the following elements is a semiconductor

A. Na

B. Ba

C. Sr

D. Ge



# **Revision Exercises Fill In The Blanks**

1. The donor energy level is close to the

# band in n type semiconductor



2. The fermi level in p type semiconductoer lies

in between ..... level and valence abnd

Watch Video Solution

**3.** On adding trivalenet impurity in a pure semiconductor the fermi level shifts very close to the ......band

**4.** The highest energy level which can be occupied by an electron in valence band at OK is known as



5. When the .....of the battery is connected to p side and negative terminal to the n side then the diode is said to be in forward bias

# 6. In forward bias the width of depletion layer

is



**7.** A circuit in which large numbr of resistor capacitors diodes transistor s are connected on a single small chip is known as.....



10. The potential harrier for Si is .....V

and for Ge is .....V

Watch Video Solution

**Revision Exercises Short Answer Question** 

1. Distinguish between intrinsic semiconductor and p-type semiconductor. Give reason, why a p-type semiconductor crystal is electrically neutral, although  $n_h > > n_e$ ?



**2.** Draw the enrgy ban diagrams of (i) n type and (ii) p type semiconductor at temperature T > 0K in the case n type Si semiconductor the donor energy level is slightly below the bottom of conduction energy level is slightly above the tip of the valence band explai what role do these energy levels play in conduction and valence bands



3. which one of the two diodes is forward

biased and which is reverse biased



**4.** The figure shows the V-I characteristic of a semiconductor diode designed to operate under revese bias



(a) identify the semiconductor diode used

(b) draw the cirucuit diagram to obtain the

given characteristics of this devics

(c ) briefly expain one use of this device

#### 5. Sketch inputs A,B and output Y from a NAND

gate from the table given below

Table		
Time	Input A	Input B
t < t1	1	1
$t_1$ to $t_2$	0	0
ty to ta	0	1
ta to ta	1	0
t4 to ts	1	1
ts to te	0	0

**6.** Explain with the help of a circuit diagram how the thickness of depletion layer in a p-n junction diode changes when it is forward biased

Watch Video Solution

7. What is a rectifier explain the working of P-N

diode as half wave rectifier

**8.** What is rectification Draw relevant circuit diagram and waveforms explain the working of p-n jucntion diode as a full wave rectifier



**9.** Name the semiconductor device that can be used to regulate an irregulation dc power supply. With the help of I-V characteristics of this device, explain its working.



10. (a) Draw a neat diagram showing forward biasing of a p-n juncitonBriefly explain its working draw it s V-I charcteristics for two different intensities of illumination

**Watch Video Solution** 

11. (a) how is a photodiode fabricated

(b) briefly explain its working draw its V-I

characteristics for two different intensities of

illumination



**12.** What is a photodiode why is it kept in reverse bias for operation while the current available in forward bias happens to be more

**13.** Describe briefly using the necessary circuit diagram the three process which take place to generate the emf in a solar cell when lights falls on ti write two important criteria required for the selection of a material for solar cell fabrication

Watch Video Solution

**14.** Describe briefly lhow light emitting diode is fabricated and expalin its working write three



diode as a voltage regulator



**18.** (a). Explains briefly with the help of a circuit diagram how V-I characteristics of a p-n junction diode are obtained in (i) forward bias, and (ii) reverse bias.

(b). A photo diode is fabricated from a semiconductor with a band gap of 2.8 EV. Can it detect wave length of 6000. nm? Justify.

Watch Video Solution

**19.** Draw the cirucit of full wave recitfier with capacitor filter also draw the input and output voltage of this circuit

20. The symbol of a diode is show in the figure



(a) the diode is a rectifier diode / photo diode / zener diode (b) draw the VI characteristics of above diode (c ) a zener diode with  $V_z=6.0V$  is sued for voltage regulation if the unregulated input is 10.0 V what is the value of series resistor R (d) what is the fundamental frequency of the ripple in a full wave rectifier cirucit operating from 50 Hz mains



**21.** Draw the graph showing the variation of current with voltage for a p-n junctin diode when the diode is (i) forward biased and (ii) reyerse biased

Watch Video Solution

**22.** A zener diode of rating 100 mW to be used as a voltage regulator if the zener ddiode has the breakdwon voltage of 5 V and it has to

regulate should be the value of  $R_S$  for safe



**23.** Draw a circuit diagram of a full-wave rectifier. Explain its working principle. Draw the input/output wave forms indicating clearly the function of the two diode used.





24. (i) three photodiodes  $D_1$ ,  $D_2$  and  $D_3$  are made of semiconductors adving band gaps of 2.5 eV 2eV and 3eV respecitvely which of them will not be able to detect light of wavelenghth 600nm

(ii) why phtoodiodes are required to operate in revese bias explain



# 25. DIFFERENCE BETWEEN VALANCE BAND,

# CONDUCTION BAND AND ENERGY BAND

Watch Video Solution

# 26. Write logic symbol boolean expression and

truth table of AND and NOR gate

27. Write logic symbol boolean expression and

truth table of NAND and OR gate

Watch Video Solution

28. Write logic symbol boolean expression and

truth table of NOT and OR gate ]

**29.** What is a logic gate name the logic gate obtained from the figure and write its truth

table



**30.** What is the equivalent circuti of the combination given below answer with proper

#### truth table



# 31. Give the truth table for the following logic

circuit



**32.** What is solar cell why are Si and Ga as preferred materials for solar cell give its V-I characteristics ]

Watch Video Solution

**33.** (a) Draw a neat diagram for a full wave rectifier circuit

(b) Draw the logic gate symbol and the truthtable for a NAND gate with tow inputs(c) In an n-p-n tranasistor circuit the collectorcurrent is 10 mA if 95% of the enemitter

current reach the collector what is the base

current



34. In the following diagram which bulb out of

 $B_1$  and  $B_2$  will glow and why



**35.** What is an integrated cirucit (IC) mention the most widely used technilogy in the fabricaton of IC



**36.** (a) Draw the V-I characteristic curve for forward and reverse bias of a p-n juction diode (b) what are th majority and ninority carriers in a p type semiconductor

(c) wirte down the symbol and truth table of

OR gate



37. (a) A student wants to use tow p-n junction
diodes to convert alternating current in to
direct curent draw the labelled circuit diagram
she would use and explain how it works
(b) give the truth table and circuit symbol for
NAND gate



#### **Revision Exercises Long Answer Questions**

 (a) distinguish between metals inlsulators and simi conductors on the baisi of their energy bands

(b) why are photodiodes used preferabley in reverse bias condlition can it detect a wavelength of 6000 nm justify


2. (i) wirte two difference among conductors semiconductor and isulator on the basic of energy band diagram
(ii) in a p-n juction diode what is the change in the width of the depletion layer when the diode is forward bias respectively

Watch Video Solution

**3.** (a) explain briefly with the help of necessary diagrams the forward and the reverse

charqcteristic cuves in the two cases

(b) A semicionductor has equal electron and holw concentration of  $6 imes10^8$  on doping with increases to  $9 imes10^{12}/m^3$ 

(i) identifty the new semiciondcutor obtained after doping

(ii) calculate the new hole concentrati9no



**4.** (a) Describe briefly with the help of a diagram the role of the two important

processes involved in the formatiojn of a p-n

junction

(b) Name the device which is used as a voltage

regulator draw the necessary cirucit diagram

and explain its working

Watch Video Solution

5. The circuit used to change alternating voltage to direct voltage is called rectifier (a) with a neat diagram explain the working of a full wave rectifier having two diodes

(b) what is the output frequency of a full wave rectifier if the input frequency is 50 Hz
(c) Draw the output waveform across the load resistance connected in the full wave rectifier circuit

Watch Video Solution

**6.** (a) Define the terms depletion layer and barrier potential for a p-n junction (i) an increase in the doping concentration and (ii) biasing across the junction affect the width of

the depletion layer

(b) Draw the circuit diagram of a p-n diode

used a s a half wave rectifier explain its working



7. (a) state briefly the processes involved in the

formation of p-n how the depletion region is

formed

(b) using the necessary circuit diagrams show

p-n junction are obtained in

(i) forward biasing (ii) reverse biasing howthese characteristic are made use of inrectification

Watch Video Solution

8. How is zener diode fabricated so as to make it a special purpose diode the significance of brekdown votlage explain brielfy with the help of a cirucit diagram how a p-n junction diode works as a half wave rectifier



**9.** identify the equivalent gate for the following cirucit and write its truth table



**10.** For CE transistor amplifier, the audio signal voltage across the collector resistance of  $2k\Omega$  is 4V. If the current amplification factor of the transistor is 100 and the base resistance is

 $1k\Omega$ , then the input signal voltage and base

current are



**11.** State the principle of working of p-n doide

as a rectifier with the help of circuit diagram

explain rdraw input and output wave forms



**Revision Exercises Numerical Problems** 

1. Find the number of acceptro atoms  $m^3$  in the silicon specimen on adding one indium atom per  $5 imes10^8$  the number density of atoms in silicon specimen is  $5 imes10^{28}$  atoms /  $m^3$ 

**Watch Video Solution** 

**2.** calculate the maximum wavelength of electromagentic radioation to create pair in germanium Energy band gap of 0.72 eV

**3.** Find the hole density in doped silicon if at  $27^{\circ}$  c the electron density and hole density are equal nd equal to  $3.0 \times 10^{16}$  on doping with arsenic electron density increases to  $9 \times 10^{19} m^{-3}$ 

Watch Video Solution

**4.** The electron concentration and hole concentration in a semicoinductor are

- $6 imes 10^{13}$  and  $7 imes 10^{13} cm^3$
- (i) what is the nature of semiconductor p type

or n type

(ii) find the resistivity of the sample if electron

mobility is 24000 and holw mobility is 200  $cm^2V^{\,-1}S^{\,-1}$ 



5. Assuming that the two diodes  $D_1$  and  $D_2$ used in the electric cirucit shown are ideal. find out the value of the current flowing

# through 1 ohm resistor



**6.** In an n-p-n transistor the base current is 1 mA if 90% of electons emitteed reach the collector then find the emitter current and collector current



. . . . . .



7. Find the curernt gain in a common base circuit if the base curent is 50  $\mu A$  emitter current is 1.2 mA

Watch Video Solution

**8.** The resistance gain and voltage gain for a commoin base amplifier are 3000 nd 2700 respectively what is the current gain and power gain of amplifier



**9.** Calculate the base current and emitter current if collector current is 6 mA and current gain is 60 in commoin emitter confitguration

Watch Video Solution

10. The internal resistance of two diodes usded in fulllwave rectifier is 20  $\omega$  (i) the

maximum and mena load current (ii) rms value

of load current



**11.** The output resistance of an n-p-n transistor is 4  $k\omega$  and input resistance is  $1k\omega$  if the current gain is 50 and output voltage is 4V then find the input voltage

Watch Video Solution

**12.** In a common base n-p-n trnsistor the current gain is 0.96 what will be the voltage gain and power gain if output resistance is 500  $k\omega$  and the input resistane is 500  $\omega$ 

Watch Video Solution

**13.** For a germanimu tansistor the change of 9 mA in emitter current produces a change of 8.8 mA in collector produce an equivalent change in base current



**14.** In n-p-n transistor 94% of the electrons reach the colectro and  $10^{12}$  electrons enter the emitter in what are the values of current transfer ratio and current amplification factor



**15.** Output characteristics of an n-p-n transistor in CE configuration is shown in the Fig. Determine



(i) dynamic output resistance (ii) dc current gain and (iii) ac current gain at an opererating point  $V_{CE}=10V$ , when  $I_B=30\mu A$ .

# > Watch Video Solution

Competion File Multiple Choice Questions With Only One Correct Answer **1.** The electrical conductivity of semicondutor increases when electromagnetic radiation of wavelength shorter than 29800 Å is incident on it. The band gap for the semiconductor is

A. 0.83 eV

B. 0.64 eV

C. 0.42 eV

D. 0.36 eV

## **Answer:**





**2.** A half wave rectifer circuit is constracted using a p-n junction dode D load resistacne R and AC source as shown below



The current thourgh R varies as





## Answer:



**3.** In the current versus voltage characteristics of a diode minimum current of 1 mA is required for the knee voltage to be is connected in a cirucit the minimum value of R

so that the voltage is above knee point is



A. 3.7 k  $\omega$ 

B. 2.3 k  $\omega$ 

C. 5.2 k  $\omega$ 

## D. 1.7 k $\omega$

# Answer:



**4.** Atoms of phosphorus aresnic indium and bismuth are used for doping pure semicondluctors to produce p type or n type semiconductors p tyhpe semocnductor

A. phosphourus arsenic indium and bismuth

B. indium and arsenic

C. phosphrous bismuth and indium

D. indium only

# Answer:



**5.** The current gain of a tramnsistor is 0.9 for common base configuration if the change in emitter current is 8 mA the change in base current is A. 0.1 mA

B. 2 mA

C. 0.8 mA

D. 1.2 mA

#### **Answer:**



6. The dominant mechanisms for motion of charge carriers in forward and reverse biased silicon P-N junction are

A. are drift and diffusion respectively

# B. are diffusin and drift respectively

C. is drift in both

D. is diffusion in both

### **Answer:**

Watch Video Solution

7. Two diodes  $D_1$  and  $D_2$  each with forward resistance of 50  $\omega$  and infinite backward resistance are connected as the current

througjh thej 150  $\omega$  resistance is



A. 1.64 A

#### B. 0.032 A

C. 0.0167 A

D. zero

#### Answer:



**8.** Four diodes are connected in the adjoining in order for the circuit toact as a full wave DC output are connected and obtained respectively across



# A. BA and CD

B. BD and AC

C. BC and AD

D. AD and BD

## Answer:

Watch Video Solution

**9.** I-V characteristics of four semiconductor devices are in graphs (i) ,(ii) (iii) and (iv) the characteristics of zener diode and solar cell are show correctly in :

1.236



A. (ii) and (iv) respectively

B. (i) and (ii) respectively

C. (ii) and (iii) respectively

D. (i) and (iv) respectively

**Answer:** 



10. In which of the following connections the

diode is forward biased



## Answer: C

**Watch Video Solution** 



The above combination of gates produces a

A. AND gate

B. XOR gate

C. NAND gate

D. NOR gate

# Answer:

Watch Video Solution

**12.** Ge and Si diods in the circuit belwo conduct at 0.3 V and 0.7 V respectiveluy if the connection of Ge diode in now reversed the change in value of V is



A. 0.2 v

B. 0.4 v

C. 0.7 v

D. 0.9 v

# Answer:



**13.** Input A,B,C,D are given to a gate and y is the oputput obtained from we can see that the gate is



A. NAND gate

B. AND gate

C. NOT gate

# D. OR gate

## Answer:

View Text Solution

**14.** Si diode used in the circuit shhas a constant voltage drop of a maximum power rating resistance R to obtain maixmum
i.

i



A. 15  $\omega$ 

B. 11  $\omega$ 

C. 17  $\omega$ 

## D. 20 $\omega$

### Answer:



15. A transistor with a current gian of  $\beta = 50$ is used as an amplifier if the voltage across the load resistance  $R_c = 5k\omega$  in the collectro cirucit is 2.5 V the base current is

A. 1 mA

B. 0.1 mA

C. 0.01 mA

## D. 0.001 mA

### Answer:

Watch Video Solution

**16.** An n-p-n tansistor circuit is show below



The arrangement represent a

A. a common - collector amplifier circuit

## B. a common - emitter amplifier circuit

C. a common - base amplifier circuit

D. a switch circuit

#### **Answer:**

Watch Video Solution

**17.** At a plate potential of 150 V the palte current in a diode is 8 mA under space charge

limited conditions if the plate potential is

## changed to 300 V the plate current is

A. 22.63 mA

B. 27.89 mA

C. 36.92 mA

D. 16.17 mA

Answer:

Watch Video Solution

**18.** In the circuit given below the p-n junction diode is ideal with negligible forward resistance and infinite backward resistance the

current in the circuit is



A. 2 mA

B. 1mA

C. 0.5 mA

#### D. zero

## Answer: D

# Watch Video Solution

**19.** In which of the following ciruict the potiential drop across the two p-n juctins are equal take all p-n junctions to be identical



A. (i) and (ii)

B. (i) and (iii)

C. (ii) and (iii)

D. only (iii)

## Answer:

Watch Video Solution

**20.** A piece of copper and anotehr piece of silicon are cooled down to 80 k from room temperatrue then the resistance of

A. copper decrease and silicon increases

B. copper increases and silicon decreases

C. both of them increases

D. both of them increases

**Answer:** 

Watch Video Solution

**21.** A Ge specimen is dopped with Al. The concentration of acceptor atoms is  $\sim 10^{21} atoms/m^3$ . Given that the intrinsic

concentration of electron hole pairs is  ${\sim}10^{19}\,/\,m^3$ , the concentration of electron in the speciman is

A.  $10^{17} \,/\, m^3$ B.  $10^{15} \,/\, m^3$ C.  $10^{12} \,/\, m^3$ 

D. 
$$10^{16}\,/\,m^3$$

### **Answer:**

Watch Video Solution

**22.** In the cirucit given below the knee voltage for both the diodes is 0.5 v the current shupplied by the battery is



A. 
$$\frac{5}{20}$$
 A  
B.  $\frac{3}{20}$  A  
C.  $\frac{5}{10}$  A  
D.  $\frac{3}{10}$  A

### Answer:



**23.** The contribution in the total current flowing through a semiconductor due to electrons and holes are  $\frac{3}{5}$  and  $\frac{2}{5}$  respectively. If the drift velocity of electrons is 2 times that of holes at this temperature, then the ratio of concentration of electrons and holes is

A. 5/2

B. 6/5

C. 5/3

D. 3/4

### Answer:

Watch Video Solution

24. In the curcuit given below  $D_1$  and  $D_2$  are two identicall diodes and V is a sinusoidal voltage source the voltage drop across the resistance  $R_L$ 



- A. is half rectified
- B. is fully rectified
- C. has same value of peak voltage for

positive and negative half cycles

D. has different value of peak voltage for

positive and negative half cycles

### Answer:



25. For the combination of gates given below

the output y is high if



A. a=0,b=1,c=0

B. A=1,B=0

C. A=0,B=0

### D. A=1,B=1

### Answer:

# Watch Video Solution

**26.** The base of a transistor is kept very thin and lightly doped as compared to the emitter and collector region so that

A. most of the carriers pass to the collector

when injected from the emitter

B. base current is high

C. recombination is increased in the bae

region

D. flow across the base region is mainly

because of majority carriers

Answer:

Watch Video Solution

**27.** A transistor -oscillator using a resonant circuit with an inductor L (of negligible resistance) and a capacitor C in series produce oscillations of frequency f. If L is doubled and C is changed to 4C, the frequency will be

A. 
$$\frac{f}{2}$$
  
B.  $\frac{f}{4}$   
C.  $\frac{f}{3}$   
D.  $\frac{f}{2\sqrt{2}}$ 

#### Answer:



**28.** For a p-type semiconductor, which of the following statements is true?

A. electrons are the majority carriers and

pentavalent atoms are the dopants

B. electrons are the majority carriers and

trivalen atoms are the dopants

C. holes are the majority carriers and

trivalen atoms are the dopants

D. holes are the majority carriers and

pendtavlent atoms are the dopants

Answer:

Watch Video Solution

29. The correct booleon operation represented

by the circuit diagram drawn is



## A. NOR

## B. AND

# C. OR

## D. NAND

## Answer:



**30.** In the energy band diagram of a material shown below, the open circles and filled circles denote holes and electrons respectively. The material is a/an



A. an inlsulator

B. a metal

C. an n type semiconductor

D. a p type semiconlductor

Answer: D

Watch Video Solution

**31.** In the circuit shown in the figure, the input voltage  $V_i$  is  $20V, V_{BE} = 0$  and  $V_{CE} = 0$ . The

values of  $I_B$ ,  $I_C$  and  $\beta$  are given by:



A.  $I_B=20\mu A, I_c=5mA, eta=250$ 

B.  $I_B=25\mu A, I_c=5mA, eta=200$ 

C.  $I_B=40\mu A, I_c=10mA, eta=250$ 

D.  $I_B=40\mu A, I_C=5mA, eta=125$ 

#### Answer:



**32.** In a p-n junction diode, change in temperature due to heating

A. does not affect resistance of p-n jucntion

B. affect only forward resistance

C. affects only reverse resistance

D. affects the overall V-I charactertics of p-n

junction

Answer: D



33. In the combination of the following gates

the output Y can be written in terms of

inputs A and B as:



A.  $\overline{A. B} + A. B$ B.  $\overline{A. B} + \overline{A}. B$ C.  $\overline{A. B}$ D.  $\overline{A + B}$ 

#### Answer:

Watch Video Solution

**34.** A light emitting diode (LED) has a voltage drop of 2V across it and passes a current of 10mA. When it operates with a 6V battery through a limiting resistor R. The value of R is

A. 40 k  $\omega$ 

B.4 k $\omega$ 

C. 200  $\omega$ 

D. 400  $\omega$ 

Answer:

**35.** A p - n photodiode is made of a material with a band gap of 2.0eV. The minimum frequency of the radiation that can be absorbed by the material is nearly

A.  $5 imes 10^{14}~{
m Hz}$ 

 $\text{B.1}\times 10^{14}~\text{Hz}$ 

 $\text{C.}~20\times10^{14}~\text{Hz}$ 

D.  $10 imes 10^{14}$  Hz

#### Answer:



**36.** A p-n photodiode is fabricated from a semiconductor with a band gap of 2.5eV. It can detect a signal of wavelength

A. 4000 nm

B. 6000 nm

C. 4000 A

D. 6000 A

#### Answer:



**37.** A transistor is operated in common emitter configuration at  $V_c = 2V$  such that a change in the base current from  $100\mu A$  to  $200\mu A$ produces a change in the collector current from 5mA to 10mA. The current gain is

A. 100

B. 150

C. 50

D. 75

#### Answer:



**38.** A common emitter amplifier has a voltage gain of 50, an input impedance of  $100\Omega$  and an output impedance of 200  $\Omega$ . The power gain of the amplifier is :-

A. 1250

B. 50

C. 500

D. 1000

Answer:

Watch Video Solution

39. If a small amount of antimony is added to

germanium crystal

A. it becomes a p type semiconductor

- B. the antimony becomes an acceptor atom
- C. there will be more free electrons than

holes in the semiconductor

D. its resistance is increased

Answer:

Watch Video Solution

**40.** Transfer characteristics vs input volage for a base biased transistor in CE configuration for using transistor as a switch it is used



A. in region I

B. in region II

C. both in region I and III

D. in region II

#### **Answer:**



**41.** C and Si both have same lattice structure, having 4 bonding electrons in each. However, C is insulator whereas Si is intrinsic semiconductor. This is because


D. the four bonding electrons in the case of

C lie in the second orbit wheras in the

case of Si they lie in the third

Answer:

Watch Video Solution

**42.** The figure shows a logic circuit with two inputs A and B and the output C. The voltage wave forms across A, B and C are as given.

# The logic circuit gate is



A. NAND gate

B. OR gate

C. NOR gate

D. AND gate



**43.** In a common emitter (CE) amplifier having a voltage gain G, the transistor used has transconductor 0.03 mho and current gain 25. If the above transistor is replaced with another one with transconductance 0.02 mho and current gain 20, the voltage gain will

A. 1.5 g

B. 
$$\frac{1}{3}$$
 g  
C.  $\frac{5}{4}$  g  
D.  $\frac{2}{3}$  g



# **44.** The ouptu x of the logic circuit will be



A. 
$$X = \overline{A.B}$$

$$\mathsf{B.}\, X = A.\, B$$

$$\mathsf{C}.\,X=\overline{A+B}$$

$$\mathsf{D}.\,X=\overline{A.\,B}$$



**45.** The given graph represents V-I characteristic for a semiconductor device

which of the following statement is correct



A. it is V-I characteristics for solar cell wher

point a reprsents open circuit voltage

and point b short circuti current

B. it is for solar cell and points a and b

represent open circuit voltage and

current repectively

C. it is for a photodiode and points a and b

represent open circuit voltage and

current respectively

D. it is for an led and points a and b

represent open circuit voltage and short

circuit current respectively

Answer:

Watch Video Solution

**46.** The barrier potential of a p-n junction depends on : (a) type of semiconductor material (b) amount of doping (c) temperature.

Which is one of the following is correct?

A. a and b only

B. b only

C. b and c only

D. a,b and c



- B.  $10^{-1}A$
- $C. 10^{-3} A$
- D. 0A



**48.** A n-p-n transisitor is connected in common emitter configuration in a given amplifier. A load resistance of  $800\Omega$  is connected in the collector circuit and the voltage drop across it is 0.8V. If the current amplification factor is 0.96 and the input resistance of the circuits is  $192\Omega$ , the voltage gain and the power gain of the amplifier will respectively be

A. 3.69,3.84

B. 4,4

### C. 4,3.69

D. 4,3.84

## Answer:

**Watch Video Solution** 

# 49. To get output 1 for the following circuit the

correct choice for the input is



C. A=1,B=0,C=1

D. A=0,B=1,C=0

#### **Answer:**

Watch Video Solution

50. The given electrical network is equivalent

to



A. AND gate

B. OR gate

C. NOR gate

D. NOT gate



**51.** In a common emitter transistor amplifier the audio signal voltage across the collector is 3V. The resistance of collector is  $3k\Omega$ . If current gain is 100 and the base resistance is  $2k\Omega$ , the voltage and power gain of the amlifier is :

A. 200 and 1000

B. 15 and 200

C. 150 and 15000

D. 20 and 2000





# Competion File Jee Main Other State Boards For Engineering Entrance

**1.** In a common emitter configuration with suitable bias, it is given that  $R_L$  is theload resistance and  $R_{BE}$  is small signal dynamic resistance (iiput side). Then, volage gain, current gain and power gain are given ,

respectively, by :

 $\beta$  is currentgain ,  $I_B, I_C$  and  $I_E$  are respectively base, collector and emitter currents.

$$\begin{array}{l} \mathsf{A.} \, \beta \frac{R_L}{R_{RE}}, \, \frac{\bigtriangleup \, I_C}{\bigtriangleup \, I_B}, \, \beta^2 \frac{R_L}{R_{BE}} \\ \mathsf{B.} \, \beta \frac{R_L}{R_{RE}}, \, \frac{tr \in \angle I_E}{\bigtriangleup \, I_B}, \, \beta^2 \frac{R_L}{R_{RE}} \\ \mathsf{C.} \, \beta^2 \frac{R_L}{R_{RE}}, \, \frac{tr \in \angle I_c}{\bigtriangleup \, I_B}, \, \beta \frac{R_L}{R_{RE}} \\ \mathsf{D.} \, \beta^2 \frac{R_L}{R_{RE}}, \, \frac{tr \in \angle I_E}{\bigtriangleup \, I_C}, \, \beta^2 \frac{R_L}{R_{RE}} \end{array}$$

### **Answer:**

Watch Video Solution

2. A common emitted amplifier circuit, built using an npn transistor, is shown in the figure. Its dc current gain is  $250, R_C = 1K\omega$  and  $V_{CC} = 10V$ . What is the minimum base current for  $V_{CE}$  to reach saturation?



A. 7  $\mu A$ 

B. 40  $\mu A$ 

# C. 10 $\mu A$

D. 100  $\mu A$ 

## Answer:

Watch Video Solution

**3.** An NPN transistor is used in common emitter configuration as an amplifier with  $1k\Omega$ load resistance. Signal voltage of 10 mV is applied across the base-emitter. This produces a 3 mA change in the collector current and  $15\mu A$  change in the base current of the amplifier. The input resistance and voltage gain are:

A. 0.67  $k\omega$  300

B. 0.67  $k\omega$  20

C. 0.33  $k\omega$  1.5

D. 0.33  $k\omega$  300



4. The reading of an ammeter for a silicon

diode in the given circuit is



A. 11.5 mA

## B. 13.5 mA

### C. 0

D. 15 mA



5. a p -n juction (D) shown in the figure can actan a rectifier An alternatting current source(V) is connected in the circuit



The corrent (I) in the resistor® can be shown

# by:





### Answer:

# **Watch Video Solution**

**6.** The logic circuit show below has the input waveform A and B as shown pick out the correct output waveform















# 7. The combination of gates shown below

yields 戻

- A. NaND gate
- B. OR gate
- C. NOT gate
- D. OR gate



**8.** The output of an OR gate is connected to both the inputs of a NAND gate. The combination will serve as a

A. NAND gate

B. NOR gate

C. AND gate

D. Or gate

Answer:

Watch Video Solution

**9.** In the givne circuit the current through zener diode is



A. 3.3 mA

B. 2.5 mA

C. 5.5 mA

D. 6.7 mA

### **Answer:**





# **10.** The I - V characteristic of an LED is.











# 11. The forward biased diode connection is







12. The currect voltage relation of diode is given by  $1 = \left(e^{1000V/T} - 1\right)mA$ , where the applied voltage V is in volt and the temperature T is in degree Kelvin. If a student makes an error measuring  $\pm 0.01V$  while measuring the current of 5mA at 300K, what will be error in the value of current in mA?

A. 0.5 mA

B. 0.05 mA

C. 0.2 mA

## D. 0.02 mA

### Answer:

# Watch Video Solution

**13.** A red LED emits light of 0.1 watt uniformaly around it. The amplitude of the electric field of the light at a distance of 1m from the diode is

A. 1.73 V/m

B. 2.45 V/m

C. 5.48 V/m

D. 7.75 V/m

## Answer:



**14.** For LEDs to emit light in visible region of

electromagnetic light it should have energy

band gap in the range of

A. 0.7 eV to 0.4 eV

B. 0.5 eV to 0.8 eV

C. 0.9 eV to 1.6 eV

D. 1.7 eV and 3.0 eV

### Answer:

Watch Video Solution

**15.** The value of the resistor  $R_s$  needed in the

DC voltage regulator circuit shown here

equals



A. 
$$\left(V_i-V_L
ight)/nI_L$$

# $\mathsf{B.}\left(V_i+V_L\right)/nI_L$

$$\mathsf{C.}\left(V_i-V_L\right)/(n+1)I_L$$

D. 
$$\left(V_i+V_L
ight)/(n+1)I_L$$

### **Answer:**



**16.** A 2 V battery is connecte across AB the value of the current supplied by the battery when in one case battery positive terminal is

connected to A and in other case when

positive terminal of battery is connected to B

will respectively be



A. 0.2 A and 0.1 A

B. 0.4 A and 0.2 A

C. 0.1 A and 0.2 A

D. 0.2 A and 0.4 A



17. A zener diode is connecte to battery and a load The currents I , $I_z$  and  $I_L$  are respectively



A. 15 mA ,5 mA ,10 mA

B. 15 mA ,7.5 mA ,7.5 mA

C. 12.5 mA ,5 mA ,7.5 mA

D. 12.5 mA ,7.5 mA ,5 mA


**18.** In an unbiased p-n junction electrons diffuse from n region to p region because

A. holes in p region attract them

B. electrons travel across the junction due

to potential difference

C. electron concentration in n region is

more as compared to that in p region

D. only electrons move forn pregion and

not the vice versa

d



**19.** if a, b, c, dare inputs to a gate and x is its output, then as per the following time graph, the gate is :

# 





## D. NAND

#### Answer:

Watch Video Solution

**20.** Identify the semiconductor devices whose characteristics are in the order (A),(b) (c ),(d)



A. simple diode zener diode solar cell light

dependent resistance

dependent resistance solar cell

C. solar cell light dependent resistance

zener diode simple diode

D. zener diode solar cell simple diode light

dependent resistance

Answer:

View Text Solution

**21.** For a common emiter configuration if a and  $\beta$  have their usualy meaning , the incorrect relationship between a and  $\beta$  is :

A. 
$$\frac{1}{\alpha} = \frac{1}{\beta} + 1$$
  
B.  $\alpha = \frac{1 - \beta}{\alpha}$   
C.  $\alpha = \frac{\beta}{1 + \beta}$   
D.  $\alpha = \frac{\beta^2}{1 + \beta^2}$ 

#### Answer:

Watch Video Solution

**22.** An experiment is preformed to determine the I - V characteristics of a Zener diode, which has a protective resistance of  $R=100\Omega$ , and maximum power of dissipation rating of 1 W. The minimum voltage range of the DC source in the circuit is :-

A. 0-5 v

B. 0-8 v

C. 0-12 v

#### D. 0-24 v

#### Answer:

# Watch Video Solution

**23.** An unknown transistor needs to be identified as npn and pnp type. A multimeter, wilth +ve and -ve terminals is used to measure resistance between different terminals transistor. If terminal 2 is the base of

the transistor then which of the following is

correct for a *pnp* transistor?

A. positive terminal 1 negative terminal 2

resistance high

B. positive terminal 2 negative terminal 1

resistance high

C. positive terninal 3 negative terminal 2

resistace high

D. positive terminal 2 negative termianl 3

resistance low



# **24.** To get an output of 1 from the circuit shown the input must be



B. a=1,b=0,c=0

C. a=1,b=0,c=1

D. a=0,b=0,c=1



**25.** A realistic graph depiciting the variation of thhe reciprocal of input resistance in an input charcteristics measurement in a com-mon emitter transistor configuration is :









# Watch Video Solution

**26.** The ratio (R) of output resistance  $r_0$  and the input resistance r, in measurements of input and output charactersitics of a transistor is typically in the range :

A. 
$$R$$
 ~  $10^2 - 10^3$ 

B.  $R \sim -1 - 10$ 

C. R~0.1-0.01

D. R~0.1-1.0

#### Answer:

Watch Video Solution

# 27. Identify the gate and match A,B,Y in bracket

to check





**28.** An n-p-n transistor has three leads A,B and C connecting B and C by moist fingers A to the positive lead of an ammeter and c to the

negative lead of the ammeter one finds large

deflection then a,b and c refer respectively to

A. emitter base and collector

B. base emitter and collector

C. base collector and emitter

D. collector emitter and base

Answer:

View Text Solution

# 29. The V-I characteristic of a diode is the ratio

of forward to revese bias resistance is



A. 10

B.  $10^{-6}$ 

 $C. 10^{6}$ 

D. 100

#### Answer:



**30.** The current gain for common emitter amplifier is 69. If the emitter current is 7.0mA, find (i) base current and (ii) collector current.

A. 9.6 mA

B. 6.9 mA

C. 0.69 mA

D. 69 mA

#### Answer:

Watch Video Solution

**31.** In a common emitter amplifier circuit using an n-p-n transistor, the phase difference between the input and the output voltages will be:-

A.  $45^{\,\circ}$ 

B.  $90^{\circ}$ 

C.  $135^{\circ}$ 

D.  $180^{\circ}$ 

#### Answer:

Watch Video Solution

**Competion File Multiple Choice Questions** 

 For an n-p-n transistor percentage of electrons emitted reaching the collector is 80% if th e collect current is 1 mA

A. the emitter current is 1.5 mA

B. the base current is 0.5 mA

C. the emitter curretn is 1.25 mA

D. the base current is 0.25 mA



**2.** To make p type semiconductor pure silicon should be doped with the impurity atoms of

A. antimony

B. boron

C. aluminum

D. inldium





**3.** In a p-n junction diode without any battery

A. there is no net charge transfer from one

region to the other

B. there is no systematic flow of charge

carriers

C. an electric field exists at the jucntion

directed from n region to p region

D. a constant electric exists near the

junction

Answer:

Watch Video Solution

4. Which of the statement is not true for a p-n

junction

A. the diffusion current in a p-n junction is

from p region to n region

B. the diffusion current in a p-n juction is

from n region to p region

C. the drift current in a p-n juction is from

n region to p region

D. the drift curretn in ap-n jucntion is from

p region to n region

#### Answer:

Watch Video Solution

**5.** A potential difference is applied across (i) an issulator at 0 k (ii) a semiconductor at 0 k (iii) a metal at 0 k (iv) a reverse biased p-n junction diode at 300 k then the current passing through

A. is zero

B. is zero

C. is inlfinite

D. is finite





# 6. Conduction through holes is not possible in

A. metals

- B. intrinsic semiconductors
- C. ionic solids
- D. p type semiconductors

Answer:



# **7.** In a common emitter amplifier circuit shown bleow if the resistance R increase then the reading of



A. ammeter decreases

B. ammeter increases

C. voltmeter increases

D. voltmeter decreases



**8.** Select the correct set of inputs and output for the given combination of logic shown below



B. A=0 ,B =1 ,Y=1



**9.** A common emitter transistor has a current amplification factor of 100 and is used as an amplifier the audio signal voltage across the collector resistance of 5 k  $\omega$  is 5 V the base resistance is 2 k  $\omega$  then

A. the input signal voltage is 0.01 v

B. the base curent is 10  $\mu A$ 

C. the input signal voltage is 0.02 v

D. the base current is 5  $\mu A$ 

Answer:

Watch Video Solution

10. A common base transistor amplifer circuit has  $200\Omega$  and  $100k\Omega$  input and ouput resistance resepectively if the current gain is 0.85 and  $I_c = 1.5$  mA then A. the voltage gain and power gain are 475

and 451 respectively

B. the base current is 0.1 mA

C. the voltage gain and power gain are 480

and 475 respectively

D. the emitter current is 160 times the base

current

Answer:

Watch Video Solution

11. Two ideal didoes are connected in a circuit

as

戻 For the circuit

A. 
$$i_i=0$$

$$\mathsf{B.}\,i_2=5mA$$

C. 
$$i_1=0.3mA$$

D. 
$$i_2=0.4mA$$

#### **Answer:**





for the combination of gates above the output

y is low where

A. A=0,B=0

B. A=1,B=0

C. A=0,B=1

D. A=1,B=1

#### Answer:



#### 13. Passage I

An n-p-n transistor is used as a voltage amplifier in a commoin emitter circuit given  $V_{\mathbb{C}} = 8VI_C = 4mA$  $V_{CE} = 4V$ ,  $(V_{BE} = 0.6V, V_{BB} = 8V$  $\beta_{Dc} = 200$ The value of load resistqacne is

A. 10 k  $\omega$ 

#### B.1 k $\omega$

C. 5 k  $\omega$ 

#### D. 2.5 k $\omega$

#### Answer:

Watch Video Solution

### 14. Passage I

An n-p-n transistor is used as a voltage amplifier in a commoin emitter circuit given  $V_{\mathbb{C}}\,=\,8VI_C=4mA$ 

 $V_{CE} = 4V,$ 

 $(V_{BE}=0.6V, V_{BB}=8V$ 

 $\beta_{Dc} = 200$ 

The value of base resistance is

A. 185 k  $\omega$ 

B. 275 k  $\omega$ 

C. 370 k  $\omega$ 

D. 410 k  $\omega$ 

Answer:


#### 15. Passage II

Diode current in a p-n junction diode is given by  $I-I_0 \left[ rac{\exp(eV)}{2kT} - 1 
ight]$  where  $I_0$  is the reverse saturation current V is the voltage across the diode k is the boltzmann constant and T is the abosolute temperatuer For a given diode  $I_0 = 5$  pA and T =300 k The forward current at a foward voltage V=0.6 V is

#### A. 0.05475 A

#### B. 0.06319 A

C. 0.04482 A

D. 0.03798 A

#### **Answer:**

> Watch Video Solution

**16.** In a p - n junction diode, the currect I can expressed as  $I = I_0 \exp\left(\frac{eV}{2k_BT} - 1\right)$  where  $I_0$  is called the reverse saturation current, V is the voltage across the diode and is positive for forward bias and negative for reverse bias,

and I is the current through the diode,  $K_B$  is the Boltzmann constant  $(8.6 \times 10^{-5} eV/K)$ and T is the absolute temperature. If for a given diode  $I_o = 5 \times 10^{-12}A$  and T = 300K, then (a) What will be the forward current at a

formward voltage of 0.6V ?

(b) What will be the increase in the current if

the voltage across the diode is increased to

0.7V ?

(c) What is the dynamic resistance?

(d) What will be current if reverse bias voltage changes from 1V to 2V ?

A. 2.48 A

#### B. 2.97 A

C. 3.03 A

D. 3.17 A

#### **Answer:**

Watch Video Solution

17. Passage II

Diode current in a p-n junction diode is given

by  $I - I_0 \left[ rac{\exp(eV)}{2kT} - 1 
ight]$  where  $I_0$  is the reverse saturation current V is the voltage across the diode k is the boltzmann constant and T is the abosolute temperatuer For a given diode  $I_0 = 5$  pA and T =300 k When the reverse bias voltage bias voltage changes from 1 v to 2 V the current will become equal to



B. *I*<sub>0</sub>

 $C. - I_0$ 

## $D. - 2I_0$

#### Answer:

# Watch Video Solution

## **Competion File Assertion Reason Type Questions**

**1.** Assertion with the increase in temperature the conductivity of intrinsic semicionductors increases

Reason The increase in temperature result in

increase in thermal energy which cause electrons to jump to the condluction energy band

A. If both asssertion and reason are correct and reason is a correct explanation of the assertion. B. if both assertion and reason are corect but reason is not the correct explanation of assertion.

C. If assertion is correct but reason is

incorrect.

D. If assertion is incorrect but reason is

correct

Answer:

Watch Video Solution

2. Assertion for the cicruit show below Y=0

when A=B=1



behaves as a NAND gate

A. If both asssertion and reason are correct

and reason is a correct explanation of

the assertion.

B. if both assertion and reason are corect

but reason is not the correct

explanation of assertion.

C. If assertion is correct but reason is incorrect.

## D. If assertion is incorrect but reason is

correct

#### **Answer:**



3. Assertion when base is thick and hightly doped the collector current is highReason When base is thick and highly doped the rate of electron hole recokbination is more

in the base region which results in larger value

of base current

A. If both asssertion and reason are correct

and reason is a correct explanation of

the assertion.

B. if both assertion and reason are corect

but reason is not the correct

explanation of assertion.

C. If assertion is correct but reason is incorrect.

## D. If assertion is incorrect but reason is

correct

#### **Answer:**

Watch Video Solution

Assertion : ohm's law is not obeyed by semiconductors
Reason the rate of flow of charge in semiconductors depends both on applied

voltage and rate of availability of charge carries

A. If both asssertion and reason are correct

and reason is a correct explanation of

the assertion.

B. if both assertion and reason are corect

but reason is not the correct

explanation of assertion.

C. If assertion is correct but reason is incorrect.

## D. If assertion is incorrect but reason is

correct

#### **Answer:**



5. Assertion : when a pure semiconductor is

doped with a trivalen impurity the number of

hols becomes more than the number of electrons

Reason Electrons get recombined with the

holes as their concentration increases on addition of trivalent impurity so number of holes become more

A. If both asssertion and reason are correct and reason is a correct explanation of the assertion.
B. if both assertion and reason are corect

but reason is not the correct

explanation of assertion.

C. If assertion is correct but reason is

incorrect.

D. If assertion is incorrect but reason is

correct

Answer:

Watch Video Solution

6. Assertion Forward bias reduces the barrier

potential

Reason : potential barrier always opposes the

applied potential

A. If both asssertion and reason are correct

and reason is a correct explanation of

the assertion.

B. if both assertion and reason are corect

but reason is not the correct

explanation of assertion.

C. If assertion is correct but reason is incorrect.

## D. If assertion is incorrect but reason is

correct

#### **Answer:**

Watch Video Solution

7. Assertion : Silicon is preferred over germanimum in preparing diodes
Reason the number of free conduction electrons is significant in Si and small in go at room temperature

A. If both asssertion and reason are correct
and reason is a correct explanation of
the assertion.
B. if both assertion and reason are corect
but reason is not the correct
explanation of assertion.
C. If assertion is correct but reason is
incorrect.
D. If assertion is incorrect but reason is

correct

#### Answer:



8. Assertion concentration of free electrons in an n type semiciondluctor is approximately equal to the density of donor atoms Reason when a p-n junction is forward biased the injected hole curent in the n region is proportional to the total charge of inljected minority carrier holes

A. If both asssertion and reason are correct
and reason is a correct explanation of
the assertion.
B. if both assertion and reason are corect
but reason is not the correct
explanation of assertion.
C. If assertion is correct but reason is
incorrect.
D. If assertion is incorrect but reason is

correct

### Answer:



**9.** Assertion In a common emitter amplifier circuit load resistance of the output circuti is 800 times the load resistance of the input if  $\alpha$  =0.95 voltgae gain of the amplifier is  $15.2 \times 10^3$ Reason  $\alpha = \frac{\beta}{1-\beta}$  where symbols have their usual meaning

A. If both asssertion and reason are correct
and reason is a correct explanation of
the assertion.
B. if both assertion and reason are corect
but reason is not the correct
explanation of assertion.
C. If assertion is correct but reason is
incorrect.
D. If assertion is incorrect but reason is

correct



# **Competion File Matching Type Questions**

**1.** Each question has a matching list the codes for the lists have choices (a) ,(b) ,(c ) and (d) out of which only one is correct



A. 
$$egin{array}{cccc} P & Q & R & S \ 1 & 2 & 3 & 4 \end{array}$$

$$\begin{array}{ccccccccccccccc} & P & Q & R & S \\ \hline 2 & 3 & 1 & 4 \\ \\ C. & P & Q & R & S \\ \hline 2 & 3 & 4 & 1 \\ \\ D. & P & Q & R & S \\ \hline 2 & 1 & 4 & 3 \end{array}$$

## Answer:

View Text Solution

**2.** Each question has a matching list the codes for the lists have choices (a) ,(b) ,(c ) and (d) out of which only one is correct



A.
$$P$$
 $Q$  $R$  $S$  $4$  $3$  $1$  $2$  $B.$  $P$  $Q$  $R$  $S$  $4$  $3$  $2$  $1$  $C.$  $P$  $Q$  $R$  $S$  $2$  $4$  $1$  $3$  $D.$  $P$  $Q$  $R$  $S$ 

#### **Answer:**

View Text Solution

**Competion File Matrix Match Type Questions** 

**1.** Each question contains statements given in two columns which are to be matched statements in column I are labelled as A,B,C and D whereas statements in column II are labelled as p,q,r and s match the entres of columnn I with appropriate entries of column II each entry in column I may have one or more than one corect option from column II the answers to these questions have to be appropriately bubbled as illustrated in the given example if the correct matches are

A 
ightarrow (q,r), B 
ightarrow (p,s)





**2.** Each question contains statements given in two columns which are to be matched statements in column I are labelled as A,B,C and D whereas statements in column II are labelled as p,q,r and s match the entres of columnn I with appropriate entries of column Il each entry in column I may have one or more

than one corect option from column II the answers to these questions have to be appropriately bubbled as illustrated in the given example if the correct matches are A 
ightarrow (q,r), B 
ightarrow (p,s) $C 
ightarrow (r,s) ext{ and } D 
ightarrow (q)$  then correctly

bubbled matrix will look like the following :





**Competion File Integer Type Questions** 

**1.** A photon of sodium light has energy equal to the band gap of a semicondluctro at room temperature T= 300 k a minimum energy E is required to generate an electron hole pair find the value of E//kT-80 close to nearest integer tke k =  $8.62 \times 10^{-15} eVK^{-1}$ 





2. At T=300 k the concentration of hole electron pairs in pure silicon is  $6 imes 10^{15}$  per cubic metre it is then doped with a pentavelent impurity contribnuting only 1 atom in  $10^7$  atoms of pure silicon olly half of the impurity atoms contribute electrons in the condluction band the number of charge carier increases by a factor of  $9x imes 10^4$  due to doping find the value of x take number of silicons atoms cubic meter  $\,=4.32 imes10^{28}$ 



**3.** An electron with a speed of  $3 \times 10^5$  m/s appraches a p-n juction having a potential barrier of 0.20 V from the n side if it enters the p side with speed v then calculate the value of  $\frac{5v}{10^5}$  close to the nearest integer



**4.** On changing the emitter current by 8.1 mA a change of 7.92 mA is observed in the colector current find the value of 100 lpha-2eta





5. The reverse saturation cureent for a p-n junction diode at  $27^{\circ}$  C is 70  $\mu A$  the forward voltage across the diode is decreased form 0.2 v to 0.15 v if the decrease in diode current is

#### expressed as

# take boltzmann constant = $8.6 imes10^{-5}$ eV/K



View Text Solution

**6.** In an n-p-n transistor  $10^{12}$  electrons cross the emitter in 10 ms when 2% of the elctrons are lost in the base the current amplification factor of the transistor is  $\beta$  if  $\beta = (5 + x)^y$ calculate  $y^x$ 







7. When forawsd biased constant voltage drop of 0.7 v and 0.3 v appeears across the Si and Ge diodes respectively calculate the difference in input in the given circuit diagram using the properties of a diode





8. The output DC voltage equal to 40 V of a half wave rectifier is supplied to a load resistance of 400  $\omega$  the value of maximum input AC voltage in half wave rectifier has a resistance of 100  $\omega$  is  $V_0$  if  $V_0 - 1 = 2^x 3^y 13^z$ find (y+z-x)



View Text Solution
9. In the circuit given below input voltage at the base resistance is 10 V also  $V_{BE}$  and  $V_{CE}$  are zero for the circuit if  $\frac{1000I_B - I_c \times \beta}{\frac{15V_0}{R_B}} = 4^x \times 10^y$ calculate the value of xy





**10.** The ratio of intrinsic carrier concentration of ge to that si at room temperature is n if 100

n +1

Take band gap of Ge =0.72 eV and band gap of

Si = 1.12 eV

Boltzmann constant = $1.38 imes 10^{-23} J K^{-1}$ 



View Text Solution

## Competion File Ncert Exemplar Problems Multiple Choice Question Type I

 The conductivity of a semiconductor increases with increase in temperature because

A. number density of free current carriers

increases

B. relaxatoin time increses

C. both number density of carriers and

relaxiation time increase

D. number density of current carriers

increases relaxation time decreased but

effect of decrease in relaxation time is

much less than increase in number

density

#### Answer:

Watch Video Solution

**2.** In the given is the potential barrier across a p-n jucntion when no battery is connecte across the junction



A. 1 and 3 both correspond to forward bias

of junction

- B.3 corresponds to forward bias of junction and 1 corresponds to reverse bias of junction
- C.1 corresponds to forward bias and 3

corresponds to reverse bias of junction

D. 3 and 1 both correspond to reverse bias

of junction



**3.** In the given figure assuming the diodes to be ideal



# A. $D_1$ is forward biased and $D_2$ is reverse biased and hence current flows form A to B

B.  $D_2$  forward biased and  $D_1$  is revese biased and hence no current flows form B to A and vice versa

C.  $D_1$  and  $D_2$  are both forward biased and

hence current flows form A to B

D.  $D_1$  and  $D_2$  are both reverse biased and

hence no current flows from A to B and

vice versa

Answer:

View Text Solution

**4.** A 220 V AC supply is connected between points A and B what will be the potential difference V across the capacitor ?



A. 220 v

B. 110 v

C. 0 v

D.  $220\sqrt{2}V$ 





- 5. Hole is
  - A. an anti pariticle of electron
  - B.a vacancy created when an electron

leaves a covalent bond

- C. absence of free electrons
- D. an artificially created particle

#### Answer:

Watch Video Solution

**6.** The output of the given circuit in the given figure



- A. would be zero at all times
- B. would be like a half wave rectifier with

positive cycles in output

C. would be like a half wave rectifier with

negative cycles in output

D. would be like that of a full wave recitifer

#### Answer:



**7.** In the circuit shown in the given figure if the diode forward voltage drop is 0.3 V the voltage difference between



A. 1.3 v

#### B. 2.3 v

C. 0

#### D. 0.5 v

#### Answer:

View Text Solution

## 8. Truth table for the given circuit is











#### Answer:

View Text Solution

Competion File Ncert Exemplar Problems Multiple Choice Question Type Ii

**1.** When an electric field is applied across a semiconductor,

A. electrons move from lower energy level to higher energy level in the conduction band B. electrons move from higher enrgy level to lower energy level in the conduction band C. holes in the valuece band move from higher energy level to lower energy level D. holes in the valence band move from lower energy level to higher energy level

#### Answer:



2. Consider an n-p-n transistor with its base emitter junction forward biased and collector base junction reverse biased . Which of the following statements are true?

A. electrons crossover form emitter to collector

B. holes move from base to collector

C. eelctrons move from emitter to base

## D. electrons form emitter move out of base

without going to the colelctoer

#### Answer:

Watch Video Solution

**3.** The below given figure shows the transfer characteristics of a biased CE transistor which of the following statement are true



A. at  $V_i=0.4$  transistor is in active state

B. at  $V_i=1$  V it can be used as an amplifer

C. at  $V_i = 0.5$  V it can be used as a switch

#### turned off

D. at  $V_i = 2.5V$  it can be used as a swithc

turned on



**4.** In a n - p - n transistor circuit, the collector current is 10mA. If 95 per cent of the electrons emitted reach the collector, which of the following statements are true ?

A. the emitter current will be 8 mA

B. the emitter current will be 10.53 mA

C. the base current will be 0.53 mA

D. the base current will be 2 mA





C. recombination of holes and electrons

has taken place

D. immobile charged ions exist



**6.** What happens during regualtion action of a Zener diode?

A. the current in and voltage across the

zener remains fixed

B. the current through the series

resistance  $R_s$  changes

C. the zener resistance is constant

D. the resistance offered by the zener

changes

#### **Answer:**



7. To reduce the ripples in rectifier circuit with

capacitor filter

A.  $R_L$  should be increased

B. input frequency should be decresed

C. input frequency should be increased

## D. capacitors with high capiacitance should

be used

#### Answer:

Watch Video Solution

**8.** The breakdown in a reverse biased p-n junction diode is more likely to occur due to

A. large velocity of the minority charge carriers if the doping concetration is small B. large velocity of the miniority charge carriers if the doping concentration is large C. strong electric field in a depletion region

if the doping concentration is small

D. strong electric field in the depletion

region if the doping concentraton is

large

#### Answer:

Watch Video Solution

## Chapter Practice Test For Board Examination

## 1. What is the behaviour of semiconductors at

room temperature



**2.** What is the phase relationship in the output and input voltage in the common base transistor amplifier.



## 3. Why a common emitter amplifier is

preferred to a common base amplifier



4. Under what condition a transistor works as

an open switch?

Watch Video Solution

**5.** What will be the input of A and B for the

Boolean expression  $\overline{(A+B)}$ .  $\overline{(A.B)} = 1$ ?

Watch Video Solution

**6.** Name the semiconductor device that can be used to regulate an irregulation dc power supply. With the help of I-V characteristics of this device, explain its working.



**7.** What is light emitting diode (LED) ? Mention two important advantages of LEDs over con-

ventional lamps.



**8.** Name the gates P and Q shown in the figure of logic circuit given below write the truth table for the combination of the gates and identify the equivalent gate





**9.** What will happen if emitter as well as collector in a transistor are forward biased?



**10.** What is rectifier explain the working of junction diode as a full wave rectifier diagram



11. Explain that a transistor can be used as a

switch.

Watch Video Solution

**12.** Using truth tables of AND gate and NOT gate show that NAND gate is an AND gate followed by a Not gate hence write the truth table of NAND gate

Watch Video Solution