



PHYSICS

BOOKS - HC VERMA PHYSICS (ENGLISH)

CAPACITORS

Sample

1. A capacitor gets a charge of $60 \mu C$ when it is connected to a

battery of emf 12 V. Calculate the capacitance of the capactor.



2. Show that the SI unit of ε_0 may be written as farad $meter^{-1}$.

Watch Video Solution

3. Calculate the capacitance of a parallel-plate capacitor having 20

cm x 20 cm square plates deparated by a distance of 1.0 mm.

Watch Video Solution				

4. Calcuate the charge on each capacitor shown in figure



5. Find the equivalent capacitance of the combination shown in

figure (31.10) between the points P and N.



6. Find the equivalent capacitance of the combination shown in

figure (31.11a) between the point P and N.



7. Find the energy stored in a capacitor of capacitance $100 \mu F$ when

it is charged to a potential difference of 20 V.



8. Two parallel plate capacitors, each of capacitance `40 muF, are connected is series. The space between the plates of one capacitor is filled with a dielectric material of dielectric constant K =4. Find the equivalent capacitacne of the system.

> Watch Video Solution

9. A parallel plate capacitor has plate area A and plate separation d.

The space betwwen the plates is filled up to a thickness x (ltd) with

a dielectric constant K. Calculate the capacitance of the system.



1. A parallel plate capacitor has plates of area `200cm^2 and separation between the plates 1.00 mm. What potential difference will be developed if a charge of 1.00 nC)(i.e., 1.00X10^(-9) C) is given to the capacitor? If the plate separation is now increased to 2.00 mm, what will be the new potential difference?



2. An isolated sphere has a capacitance of 50 pF. (a) Calculate its radius. (b) how much charge should be placed on it to raise its potential ot $10^4 V$?



3. Consider the connections shown in (a) Find the capacitance between the points A and B. (b) find the charge on the three capacitors. (c) Taking the potential at the point B to be zero, find the potential at the point D.





4. If 100 volts of potential difference is applied between a and b in

the circuit of , find the potential difference between c and d.



Watch Video Solution

5. Find the charges on the three capacitors shown in figure





6. Find the equivalent capacitance of the system shown in figure between the points a and b.



Watch Video Solution

7. Find the equivalent capacitance between the point A and B in

figure .

equivalent capacitance of the given system is

$$2C = \frac{2 C_1 C_2}{C_1 + C_2}$$

 Find the equivalent capacitance between the point A and B in figure (31-W5a).





Solution : Let us connect a battery between the points A and B. The charge distribution is shown in figure (31-W5b). Suppose the positive terminal of the battery supplies a charge +Q and the negative terminal a charge -Q. The charge Q is divided between plates α and e. A charge Q_1 goes to the plate α and the rest $Q - Q_1$ goes to the plate α . The charge Q is divided between plates α and α .



8. Twelve capacitors, each having a capacitance C, are connected to

form a cube . Find the equivalent capacitance between the

diagonally opposite corners such as A and B.



9. The nagative plate of a parallel plate capacitor is given a charge of $-20X10^{-8}C$. Find the charges appearing on the four surface of the capacitor plates.



10. Three capacitors of capacitances $2\mu F$, $3\mu F$ and $6\mu F$ are connected in series with a 12 V battery. All the connecting wire are disconnected, the three positive plates are connected together and the three negative plates are connected together. Find the charges on the three capacitors after the reconnection.

Watch Video Solution

11. The connnections shown in figure are established with the swithc S open. How much charge will flow through the switch if it is closed?



12. Each of the three plates shown in figure has an area of 200 cm² on one side and the gap between the adjacent plates is 0.2 mm. The emf of the battery is 20V. Find the distribution of charge on various surfaces of the plates. What is the equivalent capacitance of the system between the terminal points?



Watch Video Solution

13. Find the capacitance of the infinite ladder shown in figure.





14. Find the energy stored in the electirc field produced by a metal

sphere of radius R containing a charge Q.



15. A capacitor of capacitance C is charged by connecting it to a battery of emf epsilon. The capacitor is now disconnected and

reconnected to the battery with the polarity reversed. Calculate the heat developed in the connecting wires.



16. An uncharged capacitor is connected to a battery. Show that half the energy supplied by the battery is lost as heat while charging the capacitor.

Watch Video Solution

17. A parallel-plate capacitor having plate are $100cm^2$ and separation 1.0 mm holds a charge of $0.12\mu C$ when connected to a 120 V battery. Find the dielectric constant of the material filling the gap.

18. A parallel plate capacitor is formed by two plates, each of area $100cm^2$, separated by a distance of 1 mm. A dielectric of dielectric constant 5.0 and dielectric strength $1.9X10^7Vm^{-1}$ is filled between the plates. Find the maximum charge that can be stored on the capacitor without causing any dielectric breakdown.



19. The space between the plates of a parallel plate capacitor of capacitance C is filled with three dielectric slabs of identical size as shown in figure. If the dielectric constants of the three slabs are

 K_1, K_2 and K_3 find the new capacitance.



20. Figure shown a parallel-plate capacitor having square plates of edge a and plate-separation d. The gap between the plates is filled with a dielectric of dielectric constant K which varies parallel to an edge as where K and a are constants and x is the distance from the

left end. Calculate the capacitance.



21. A parallel plate capacitor of capacitance `100 microfarad is connected a power supply of 200 V. A dielectric slab of dielectric constant 5 is now inserted into the gap between the plates. (a) Find the extra charge flown through the power supply and the work done by the supply. (b) Find the change in the electrostatic energy of the electric field in the capacitor.



22. Shown a parallel plate capacitor with plates of width b and length l. The separation between the platesis d. The plates are rigidly clamped and connected to a battery of emf V. A dielectric slab of thickness d and dielectric constant K is slowly inserted between the plates. (a) Calculate the energy of the system when a length x of the slab is introduced into the capacitor. (b) what force should be applied on the slab to ensure that is goes slowly into the capacitor? Neglect any effect of friction or gravity.



23. A parallel-plate capacitor is placed in such a way that its plates are horizontal and the lower plate is dipped into a liquid of

dielectric constant K and density ρ . Each plate has an area A. The plates are now connected to a battery which supplies a positive charge of magnitude Q to the upper plate. Find the rise in the level of the liquid in the space between the plates. (figure)





Objective 1

1. A capacitor of capacitance C is charged to a potential V. The flux of the electric field through a closed surface enclosing the capacitor is

A.
$$\frac{CV}{\varepsilon}$$

B. $\frac{2CV}{\varepsilon_0}$
C. $\frac{CV}{2es\psi lon_0}$

Answer: D



A. $2C \,$ and $\, 2V$

B. 2C and 2V

 $\mathsf{C}.\,2C$ and V

 $\mathsf{D.}\ 2C \ \text{and} \ V$

Answer: D



3. If the capacitors in the previous question are joined in parallel,the capacitance and the breakdown voltage of the combination will be

A. $2C \,$ and $\, 2V$

 $\mathsf{B.}\,C \ \text{and} \ 2V$

 $\mathsf{C.}\,2C$ and V

 $\mathsf{D}.\,C \ \text{and} \ V$

Answer: C



4. The equivalent capacitance of the combination show in figure is



A. C

 $\mathsf{B}.\,2C$

$$\mathsf{C}.\left(\frac{C}{2}\right)$$

D. none of these

Answer: B



5. When a dielectric slab is gradually inserted between the plates of an isolated parallel-plate capacitor , the energy of the system decreases.What can you conclude about the force on the slab exerted by the electric field?

A. increase

B. decrease

C. remain unchangeed

D. become zero

Answer: C



6. The energy density in the electric fieled created by a point change falls off with the distanse from the point charge as

A.
$$\left(\frac{1}{r}\right)$$

B. $\left(\frac{1}{r^2}\right)$
C. $\left(\frac{1}{r^3}\right)$
D. $\left(\frac{1}{r^4}\right)$

Answer: D



7. A parallel-plate capacitor has plates of unequal area . The larger plates is connected to the positive terminal of the battery and the smaller plate to its nagative terminal. Let Q+ and Q-be the charges appearing on the positive and negative plates respectively

A.
$$Q_+\,>Q_-$$

$$\mathsf{B.}\,Q_{\,=}\,Q_{\,-}$$

 $\mathsf{C}.\,Q_+\,< Q\,-$

D. The information is not sufficient to decide the ralation between Q_{\pm} and Q_{\pm}

Answer: B

Watch Video Solution

8. A thin metal plate P is inserted between the plates of a parallel-

plate capacitor of capacitance C in such a way that its edges touch

the two plates (figure 31-Q2). The capacitance now becomes.



A.
$$\left(\frac{C}{2}\right)$$

 $\mathsf{B.}\,2C$

C. 0

D. indeterminated

Answer: D

Watch Video Solution

9. Figure show two capacitors connected in series and joind to a bettery. The graph shows the variation in potential as one movies from left to right on the branch containing the capacitors.



D. The information is not sufficient to decide the ralation

between Q_+ and $Q_.$

Answer: C

Watch Video Solution

10. Two metal plates having charges Q and -Q face each other at some separation and are dipped into an oil tank .If the oil is pumped out, the eletric field between the plates will

A. increase

B. decrease

C. remain unchangeed

D. become zero

Answer: A

Watch Video Solution

11. Two metal spheres of capacitances C_1 and C_2 carry some charges . They are put in contact and then seperated. The final charges Q_1 and Q_2 on them will satisfy

A.
$$\frac{Q_1}{Q_2} < \frac{C_1}{C_2}$$

B. $\frac{Q_1}{Q_2} = \frac{C_1}{C_2}$
C. $\frac{Q_1}{Q_2} > \frac{C_1}{C_2}$
D. $\frac{Q_1}{Q_2} = \frac{C_2}{C_1}$

Answer: B



12. Three capacitors of capacitances $6\mu F$ each are available. The minimum and maximum capacitances, which be obtained are

A. $6\mu F$, $18\mu F$

B. $3\mu F$, $12\mu F$

 $\mathsf{C.}\,2\mu F,\,12\mu F$

D. $2\mu F$, $18\mu F$

Answer: D Watch Video Solution

Objective 2

1. The capacitance of a capacitor does not depend on

A. the shape of the plates

- B. the size of the plates
- C. the charges on the plates
- D. the separation between the plates

Answer: C



2. A dielectric slab is inserted between the plates of an isolatted charged capacitor. Which of the following quantities will remain the same?

A. The electric field in the capacitor

B. The charge on the capacitor

C. The cpotential difference between the plates

D. The stored energy in the capacitor

Answer: B



3. A dielectric slab is inserted between the plates of a capacitor. The charge on the capacitor is Q and the magnitude of the induced charge on each surface of the dielectric is Q'. A. Q' may be larger than Q.

- B. Q' must be larger than Q.
- C. Q' must be equal to Q.
- D. Q'must be smaller tha Q.

Answer: D



4. Each plate of a parallel plate capacitor has a charge q on it. The capacitor is now connected to a battery. Now,

A. the facing surfaces of the capacitor have equal and opposite

charges

B. the two plates of the capacitor have equal and opposite

charges

C. the battery supplies equal and opposite charges to the two

plates

D. the outer surfaces of the plates have equal charges

Answer: A::C::D

Watch Video Solution

5. The separation between the plates of a charged parallel-plate capacitor is increased. Which of the following quantities will change?

A. Charge on the capacitor

B. potential difference across the capacitor

C. Energy of the capacitor

D. Energy density between the plates

Watch Video Solution

6. A parallel-plate capacitor is connected to a battery. A metal sheet of negligible thickness is placed between the plates. The sheet remains parallel to the plates of the capacitor.

A. The battery will supply more charge.

B. The capacitance will increase.

C. The potential difference between the plates will increase.

D. Equal and opposite charges will appear on the two faces of

the metal plate.

Answer: D

1. When $1.0 imes 10^{12}$ electrons are transferred from one conductor to another, a potential difference of 10V . What will be capacitance of the two -conductor system .



2. The plates of a paraller-plate capacitor are made of circular discs of radii5.0cm each .If the separation between the plates is 1.0 mm,What is the capacitance?



3. Suppose ,one wishes to construct a1.0farad capacitor using circular discs. If the separaton between the discs be kept at 1.0mm, what would be the rradius of the discs?



4. A parallel -plate capacitor having plate area `25cm^2 and separation 1 mm is connected to a battery of 6 V.. Calculate the charge flowing through the battery . How much work has been done by the battery during the process ?

Watch Video Solution

5. A parallel -plate capacitor having plate area 25.0cm² and a separation 2.00mm between the plates .the capacitor is connected to a bettery of 12.0V.(a)find the charge on the capacitor .(b) the
plate separation is decrerased to 1.00mm. Find the extra charge given by the bettery to the positive plate.



6. Find the charges on the three capacitors connected to a bettery as shown in figure (31.E1). Take `C_1=2.0,muF, C_2=4.0,muf, C_3=6.0,muF and V=12 volts.





7. Three capacitors having capanctances $20\mu F, 30\mu F$ and $40\mu F$ are conneceted in series with a 12V battary. Find the charge on

each of the capacitors. How much work has been done by the battery in charging the capacitors?



8. Find the charges on the three capacitors connected to a bettery

as shown in figure (31.E1). Take $C_1 = 2.0 = 2.0, \, \mu F, \, C_2 = 4.0, \, \mu f, \, C_3 = 6.0, \, \mu F \, \, {\rm and} \, \, V = 12 vo < s$.(31-E1). Take

 $C_1 = 2.0 \mu F, C_2 = 4.0 \mu F, C_2 = 6.0 \mu F \,\, {
m and} \,\, V = 12 vo < s.$



Watch Video Solution

9. Take $C_1 = 4.0 \mu F$ and $C_2 = 6.0 \mu F$ in figure. Calculate the equivalent capacitance of the combination between the point s indicated.





10. Find charge supplied by the bettery in the arrangement shown

in figure.



11. The outer cylinders of two cylindrical capacitors of capacitance 2.2 microFarad each , are kept in contact and the inner cylinders are connected through a wire .A battery of end 10V is connected as shown in figure. Find the totatl charge supplied by the bettery to

the inner cylioders.



12. Two conducting spheres of $\operatorname{rad}_{i} R_{1}$ and R_{2} are kept widely separated from each other . What are their individual capacitances? **13.** Each of the capacitors shown n figure has a capacitance of 2 microFarad . Find the equivalent capacitance of the assembly between the points A and B . Suppose ,a battery of end of emf 60 volts is is connected between A and B .Find the potential difference appearing on the individual capacitors .





14. It is required to consttruct a 10 mu F capacitor which can be connected across a 200V bettery . Capacitance 10 mu F are available but they can withstand only 50V ,Degin a combination which can yield the desired result .

Watch Video Solution

15. Take the potential of the point B in figure to be zero . (a) Find the potentials at the points C and D ,(b)If a capacitor is connected between C and D , what charge will appear on the capacitor ?





17. A capacitor is made of a flat plate of area A and a second plate having a stair -like structure as shown in figure. The width of each

Watch Video Solution

stair is a and the height is b. Find the capacitance of the assembly.



18. A cylindrical capacitor is constructed using two coaxial cylinders of the same length 10cm of radii 2mm and 4mm. (a) calculate the capacitance (b) another capacitor of the same length is constructed with cylinders of radii 4mm and 8mm. Calculate the capacitance . **19.** A $100\mu F$ capacitor is charged to a potential difference of 24V. It is connected to an uncharged capacitor of capacitance $20\mu F$ What will be the new potential difference across the $100\mu F$ capacitor?

Watch Video Solution

20. Each capacitor shown in figure has a capacitance of 5.0 mu F ,

The emf of the battery is 50 V, How much charge will flow though

AB if the switch S is closed ?

Watch Video Solution

21. The particle P shown has a mass of 10mg and a charge of

 $-0.01 \mu C$. Each plate has a surface area





22. Both the cacpacitors shown in figure are made ofsquare of edge a The separations between the plates of the capacitors are d_1and d_2as shown in the figure A potential difference V is applied between the point a and b .An electron is projected between the plate s of the upper capacitor along the central line . With what minimum speed should the electron be projected so that it is does

not collide with any plate ? consider only the electric forces.



23. The plate of a capacitor are 2.00cm apart . An electron -proton pair is released somewhere in the gap between the plates and it is found that the proton reaches the negative plate . At what distance from the negative plate was the pair released?



24. Convince yourself that parts (a) ,(b) and (c) of figure are identical . Find the capaciance between the point A and B of the assembly .



25. Find the potential difference $V_a - V_b$ between the points a and b shown in each part of the figure.



26. Find the equivalent capacitances of the combinations shown in

figure between the indicated points.



27. Find the capacitance of the combination shown in figure between A and B .

between the indicated points.



View Text Solution

28. Find the equivalent capacitance of the point A and B .



29. An infinite ladder is constructed by connecting several sections of $2\mu F$, $4\mu F$ capacitor combinations as shown in figure . It is terminated by a capacitor of capacitance C . What value should be chosen for C, such that the equivalent capacitance of the number

of sections in between ?



30. A charge of $+2.0 \times 10^{-8}C$ is placed on the positive plate and a charge of -2.0x10 ^-8 C at negative plate. And capacitance of capacitor is 1.2 x (10^-3) mu F. Calculate the potential difference developed between the plates.



31. A charge of 20 microCoulomb is placed on the positive plate of on isolated parallel - plate capacitor of capacitance 10microFarad calculate the potential difference developed between the plates .



32. A charge of $1\mu C$ is given to one plate of a parallel - plate capacitor of capacitance $0.1\mu F$ and a charge of $2\mu C$ is given to the other plate . Find the potential difference developed between the plate .

Watch Video Solution

33. Each of the plates shown in figure (31-E19) has serface area $\left(\frac{96}{\varepsilon_0}\right) \times 10^{-12}$ Fm on one side and the seperation between the consecutive plates is 4.0 mm. The emf of the bettery connected is `10 volts . Find the magnitude of the charge supplied by the bettery

to each of the plates connected to it .



34. The capacitance between the adjacent plates shown in figure (31-E20) is 50nF. A charge of $1.0\mu C$ is placed on the middle plate (a) What will be the charge on the outer surface pf the upper plate ? (b) Find the potential difference developed between the upper

and the middle plates .
Vatch Video Solution

35. Consider the situation of the given figure . If $1.0\mu C$ is placed on the upper plate , what will be the potential difference between (a) the upper and middle plates and (b) the middle and the lower plate? If capacitance of each capacitor is 50 nF.

Watch Video Solution

36. Two capacitors of capacitances 20.0pF and 50.0pF are connected in series with a `6.00V bettery . Find (a)the potential

difference across each capacitor and (b) the energy stored in each

capacitor.

Watch Video Solution

37. Two capacitor of capacitance $4.0\mu F$ and `6.0muF' are connected in series with a battery of 20 V . Find the energy supplied by the battery .

Watch Video Solution

38. Each capacitor in figure has a capaciance of $10\mu F$. The emf of the bettery is 100V . Find the energy stored in each the four







39. A capacitor with stored energy 4.0J is connected with an identical capacitor with no electric field in between . Find the total energy stored in the two capacitors .



40. A capacitor of capacitor of capacitance $2.0\mu F$ is charge to a potential diffrence of 12V It is then connected of uncharged capacitor of capacitance $4.0\mu F$ as shown in figure . Find (a) the charge on each of the two capacitors after the connection, (b) the electrostatic energy stored in each of the two capacitors.



Watch Video Solution

41. A point charge Q is placed at the origin . Find the electrostatic

energy stored outside the sphere of radius R centred at the origin.

Watch Video Solution

42. A metal sphere of radius R is charged to a pontital V . (a) Find the electrostatic energy stored in the electric field within a concentric sphere of radius 2 R . (b)Show that the electrostatic field energy stored outside the sphere of radius 2R equals that stored within it .



43. A large conducting plane has a surface charge density $1.0 \times 10^{-4} Cm^{-2}$. Find the electrostatic energy stored in a cubical volume of edge 1 cm in the front plane.



44. A parallel - plate capacitor having plate area $20cm^2$ and seperation between the plates 1.00mm is connected to a battery of

12.0V. The plates are pulled apart to increase the separation to 2.0mm. (a) calculate the charge flown through the circuit during the process . (b) How much energy is absorbed by the battery during the process ? (c) calculate the stored energy in the electric field before and after the process . (d) Using the expression for the force between the plates , find the work done by the person polling the plates apart . (e) Show and justify that no heat is produced during this transfer of charge as the separation is increased.

Watch Video Solution

45. A capacitor having a capacitance of $100\mu F$ is charged to a potential difference of 24V. The charging battery is disconnected and the capacitor is connected to another battery of emf 12V with the positive plate of the capacitor joined with the positive terminal of the battery. (a) Find the charges on the capacitor before and after the reconnection. (b) Find the charge flown through the 12V

battery . (c) Is work done by the battery or is it done on the battery ? find its magnitude . (d) Find the decrease in electrostatic field energy . (e) Find the best developed during the flow of charge after reconnection.

Watch Video Solution

46. Consider the situation shown in figure (31-E23). The switch S is open for a long time and then closed. (a) Find the charge flown through the battery when the switch S is closed (b)Find the work done by the battery.





47. A capacitor of capacitor $5.00\mu F$ is charged to 24.0V and another capacitor of capacitance $6.0\mu F$ is charged to 12.0V (a) Find the energy stored in each capacitor .(b)The positive plates of the first capacitor is now connected to the negative plate of the second and vice versa . Find the new charges on the capacitors . (c)Find the loss of electrostatic energy during the process . (d)Where does this energy go?



48. A $5.0\mu F$ capacitor is charged to 12V. The positive plate of this capacitor is now connected to the negative terminal of a 12V battery and vise versa . Calculate the heat developed in the connecting wires.

49. The two square faces of a rectangular dielectric slab (dielectric constant4.0) of dimensions 20cm x20cm x 1.0mm are metal -coated. Find the capacitance between the coated surfaces.

Watch Video Solution

50. If the above capacitor is connected across a 6.0V battery, find (a)the charge supplied by the battery, (b)the induced charge on the dielectric and (c)the net charge appearing on one of the coated surfaces.



51. The separation between the plates of a parallel-plate capacitor is 0.500 cm and its plate area is $100cm^2$. A 0.400cm thick metal

plate is inserted into the gap with its faces parallel to the plates .Show that the capacitance of the assembly is independent of the position of the metal plate within the gap and find its value.



52. A capacitor stores $50\mu c$ charge when connected across a battery. When the gap between the plates is filled with a dielectric , a charge of `100muc flows through the battery .Find the dielectric constant of the material inserted.



53. A parallel-plate of capacitor of capacitance $5\mu F$ is connected in a battery of emf 6V. The separation between the plate is 2mm.(a) Find the charge on the positive plate.(b) find the eletric field between the plate.(c) A dielectric slab of thickness 1 mm and dielectric constant 5 is inserted into the gap to occupy the lower half of it.Find the capacitance of the new combination .(d)How much charge has flow n through the battery after the slab is inserted?

Watch Video Solution

54. A paller- plate capacitor has plate area $100cm^2$ and plate separation 1.0cm.A glass plate (dielectric constant 4.0)are inserted one over the other the fill the space between the plate of the capacitor.Find the new capacitance.

Watch Video Solution

55. A parallel -plate capacitor having plate area $400cm^2$ and separation between the plate 1.0mm is connected to a power supply of 100V. A dielectric slab of thickness1.0mm and dielectric

constant 5.0 is inserted into the gap .(a)Find the increase in electrostatic energy .(b) If the power supply is now disconnected and the dielectric slab is taken out , find the further increase in energy. (c) Why does the energy increase in inserting the slab as well as in taking it out?

Watch Video Solution

56. Find the capacitances of the capacitance of the capacitors shown In figure .The plate area is *A* and the separation between the plate is *d*. Different dielectric slabe in a particular part of the figure area of the same thickness and the entire gap between the plate is filled with the dielectric slabs.



57. A capacitor is formed by two square metal plate of edge a, separated by a distance d.Dielectric constants K_1 and K_2 are filled in the gap as shown in figure(31-E25). Find the capacitance.



58. Figure shows two indentical pallel plate capacitors connected to a switch S. Initially ,the switch is closed so that the capacitors are completely charged .The switch is now opened and the free space between the plates of the capacitors is filled with a dielectric of dielectric constant 3. Find the ratio of the initial total energy

stored in the capacitors to the final total energy stored.





59. A parallel - plate capacitor of plate area A and plate separation d is charged to a potential difference V and then the battery is disconnected . A slab of dielectric constant K is then inserted between the plate of the capacitor so as to fill the space between the plate .Find the work done on the system in the process of inserting the slab.



60. A capacitor having a capacitance of $100\mu f$ is changed to a potential difference of 50V. (a) What is the magnitude of the charge on each plate? (b)The charging battery is disconnected and a dielectric of dielectric constant 2.5 is inserted . Calculate the new potential difference between the plate .

Watch Video Solution

61. A sphercial capacitor is made of two conducting spherical shells of radii a and b.The space between the shells is filled with a dielectric constant Kup to a radius c as shown in figure. Calculate





62. Suppose the space between the two inner shells of the previous problum is filled with a dielectric constant K. Find the capacitance

of the system between A and B.



63. An air -filled parallel-plate capacitor is to be constructed which can store $12\mu C$ of charge when operated at 1200V. What can be the minimum plate area of the capacitor? The dielectric strength air is $3 \times 10^6 V m^{-1}$.
64. A parallel -plate capacitor with the plate area $100cm^2$ and the separation between the plate 1.0cm is connected across a battery of emf 24 volts .Find the force of attraction between the plates.

Watch Video Solution

65. Concider the situation shown in figure .The width of each plate is b.The capacitor plates are rigidly clamped in the laboratory and connected to be a battery of emf ε All surfaces are frictionless .Calculate the value of M for which the dielectric slab will stay in

equilibrium.



Short Answer

1. Suppose a charge $+Q_1$ is given to the positive plates and a charge $-Q_2$ to the negative plate of a capacitor. What is the "charge on the capacitor"?

Watch Video Solution

2. As $C = \left(rac{1}{V}
ight) Q$, can you say that the capacitorC is proportion

to the charge Q?



3. A solid and a hollow metal spheres are given equal charges, which one will have higher electric potential.

Watch Video Solution

4. The plates of a parallel-plate capacior are given equal positive charges .What will be the potential difference between the plates ? What will be the charges on the facing surfaces and on the outer surfaces ?



5. A capacitor has capacitance C. Is this information sufficient to know what maximum charge the capacitor can contain? If yes, what is this charge? If no, what other information is needed?



.Explain this in term of polarization of the material.



7. A dielectric slab is inserted between the plates of an isolated

capacitor. The force between the plates will

Watch Video Solution