



## PHYSICS

### NCERT - NCERT PHYSICS(TELUGU)

#### ELECTRICITY

#### Examples

1. A current of 0.5 A is drawn by a filament of an electric bulb for 10 minutes. Find the amount of electric charge that flows through the circuit.



Watch Video Solution

2. How much work is done in moving a charge of 2 C across two points having a potential difference 12 V?



[Watch Video Solution](#)

3. (a) How much current will an electric bulb draw from a 220 V source, if the resistance of the bulb filament is  $1200 \Omega$ ? (b) How much current will an electric heater coil draw from a 220 V source, if the resistance of the heater coil is  $100 \Omega$ ?



[Watch Video Solution](#)

4. The potential difference between the terminals of an electric heater is 60 V when it draws a current of 4 A from the source. What current will the heater draw if the potential difference is increased to 120 V?



[Watch Video Solution](#)

5. Resistance of a metal wire of length 1 m is  $26 \Omega$  at  $20^\circ \text{C}$ . If the diameter of the wire is 0.3 mm, what will be the resistivity of the metal at that temperature? Using Table 12.2, predict the material of the wire.



[Watch Video Solution](#)


6. A  $4\ \Omega$  resistance wire is doubled on it. Calculate the new resistance of the wire.



[Watch Video Solution](#)

7. An electric lamp, whose resistance is  $20\ \Omega$ , and a conductor of  $4\ \Omega$  resistance are connected to a  $6\ \text{V}$  battery (Fig. 12.9). Calculate (a) the total resistance of the circuit, (b) the current through the circuit, and (c) the potential difference across the electric lamp and

conductor.

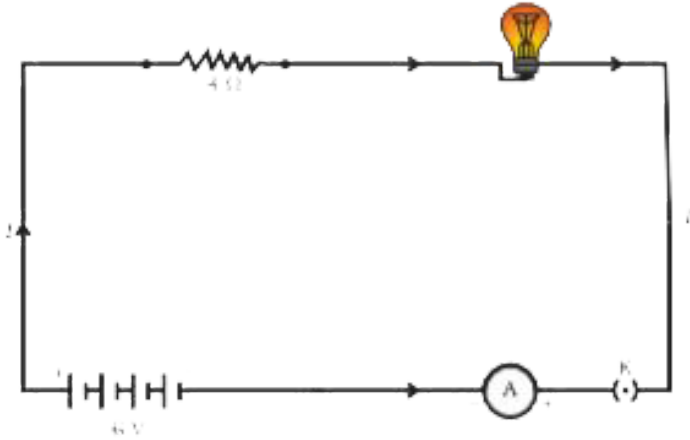

[Watch Video Solution](#)

8. In the circuit diagram given in Fig. 12.10, suppose the resistors  $R_1$ ,  $R_2$  and  $R_3$  have the values  $5\Omega$ ,  $10\Omega$ ,  $30\Omega$ , respectively, which have been connected in parallel to a battery of 12 V. Calculate (a) the current through each resistor, (b) the total

current in the circuit, and (c) the total circuit resistance.



[Watch Video Solution](#)


9. If in Fig. 12.12,

$$R_1 = 10\Omega, R_2 = 40\Omega, R_3 = 30\Omega, R_4 = 20\Omega, R_5 = 60\Omega$$

, and a 12 V battery is connected to the arrangement.

Calculate (a) the total resistance in the circuit, and (b)

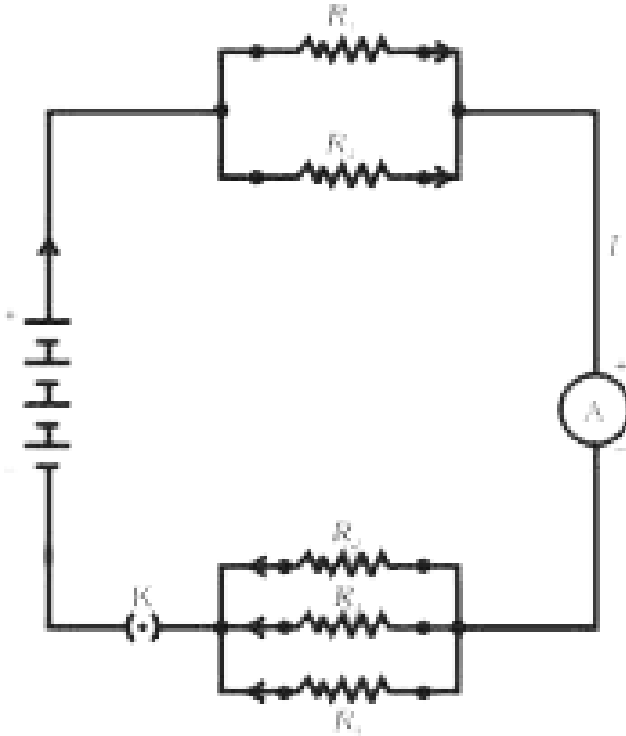the total current flowing in the circuit.



[Watch Video Solution](#)

**10.** An electric iron consumes energy at a rate of 840 W when heating is at the maximum rate and 360 W

when the heating is at the minimum. The voltage is 220 V. What are the current and the resistance in each case?



[Watch Video Solution](#)

**11.** 100 J of heat are produced each second in a  $4 \Omega$  resistance. Find the potential difference across the resistor.



[Watch Video Solution](#)

**12.** An electric bulb is connected to a 220 V generator. The current is 0.50 A. What is the power of the bulb?





[Watch Video Solution](#)

**13.** An electric refrigerator rated 400 W operates 8 hour/day. What is the cost of the energy to operate it for 30 days at Rs 3.00 per kW h?



[Watch Video Solution](#)

## Question

**1.** what does an electric circuit mean ?



[Watch Video Solution](#)

2. Define the unit of current.



**Watch Video Solution**

3. Calculate the number of electrons constituting one coulomb of charge.



**Watch Video Solution**

4. Name a device that helps to maintain a potential difference across a conductor.



**Watch Video Solution**

5. What is meant by saying that the potential difference between two points is 1 V?

 [Watch Video Solution](#)

6. How much energy is given to each coulomb of charge passing through a 6 V battery?

 [Watch Video Solution](#)

7. On what factors does the resistance of a conductor depend?

 [Watch Video Solution](#)

8. Will current flow more easily through a thick wire or a thin wire of the same material, when connected to the same source? Why?



[Watch Video Solution](#)

9. Let the resistance of an electrical component remains constant while the potential difference across the two ends of the component decreases to half of its former value. What change will occur in the current through it?



[Watch Video Solution](#)

**10.** Why are coils of electric toasters and electric irons made of an alloy rather than a pure metal?



**Watch Video Solution**

**11.** Which metal is the best conductor of electricity?




**Watch Video Solution**

**12.** Draw a schematic diagram of a circuit consisting of a battery of three cells of 2 V each, a 5  $\Omega$  resistor,

an  $8\ \Omega$  resistor, and a  $12\ \Omega$  resistor, and a plug key, all connected in series.

 [Watch Video Solution](#)

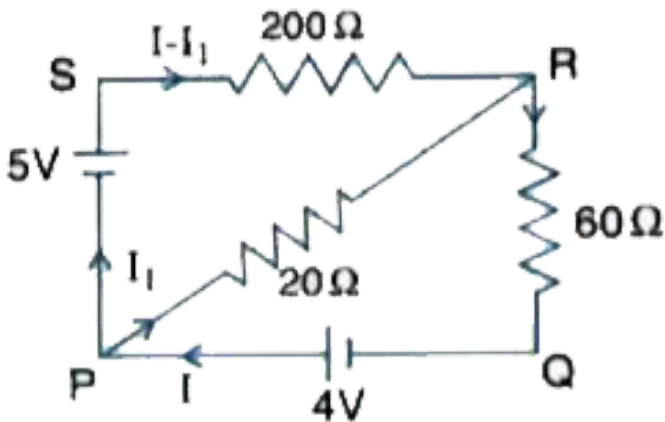**13.** In the given circuit , the two cells have no internal resistance. Calculate the potential difference across the  $20\ \Omega$  resistor .



 [Watch Video Solution](#)

**14.** Judge the equivalent resistance when the following are connected in parallel – (a)  $1\ \Omega$  and  $10^6\ \Omega$ , (b)  $1\ \Omega$  and  $10^3\ \Omega$ , and  $10^6\ \Omega$ .



**Watch Video Solution**

**15.** An electric lamp of  $100\ \Omega$ , a toaster of resistance  $500\ \Omega$ , and a water filter of resistance  $500\ \Omega$  are connected in parallel to a  $220\ \text{V}$  source. What is the resistance of an electric iron connected to the same source that takes as much current as all three appliances, and what is the current through it?



**Watch Video Solution**

 [Watch Video Solution](#)

16. What are the advantages of connecting electrical devices in parallel with the battery instead of connecting them in series?

 [Watch Video Solution](#)

17. How can three resistors of resistances  $2\Omega$ ,  $3\Omega$ , and  $6\Omega$  be connected to give a total resistance of (a)  $4\Omega$ , (b)  $1\Omega$ ?

 [Watch Video Solution](#)



**18.** What is (a) the highest, (b) the lowest total resistance that can be secured by combinations of four coils of resistance  $4\Omega$ ,  $8\Omega$ ,  $12\Omega$ ,  $24\Omega$ ?



**Watch Video Solution**

**19.** Why does the cord of an electric heater not glow while the heating element does?



**Watch Video Solution**

**20.** Compute the heat generated while transferring 96000 coulomb of charge in one hour through a

potential difference of 50 V.



[Watch Video Solution](#)

**21.** An electric iron of resistance  $20 \Omega$  takes a current of 5 A. Calculate the heat developed in 30 s.



[Watch Video Solution](#)

**22.** What determines the rate at which energy is delivered by a current?



[Watch Video Solution](#)

23. An electric motor takes 5 A from a 220 V line. Determine the power of the motor and the energy consumed in 2 h.



Watch Video Solution

## Exercises

1. A piece of wire of resistance  $R$  is cut into five equal parts. These parts are then connected in parallel. If the equivalent resistance of this combination is  $R'$ , then the ratio  $R/R'$  is –

A.  $1/25$

B.  $1/5$

C. 5

D. 25

**Answer:**



**Watch Video Solution**

2. Which of the following terms does not represent electrical power in a circuit?

A.  $i^2 R$

B.  $IR^2$

C.  $VI$

D.  $V^2 / R$

**Answer:**



**Watch Video Solution**

3. An electric bulb is rated 220 V and 100 W. When it is operated on 110 V, the power consumed will be –

A. 100 w

B. 75 W

C. 50 W

D. 25 w

**Answer:**



**Watch Video Solution**

4. Two conducting wires of the same material and of equal lengths and equal diameters are first connected in series and then parallel in a circuit across the same potential difference. The ratio of heat produced in series and parallel combinations would be –

A. 1 : 2

B. 2:1

C. 1:4

D. 4:1

**Answer:**



**Watch Video Solution**

5. How is a voltmeter connected in the circuit to measure the potential difference between two points?



**Watch Video Solution**

6. A copper wire has diameter 0.5 mm and resistivity of  $1.6 \times 10^{-8} \Omega \text{ m}$ . What will be the length of this wire to make its resistance  $10 \Omega$ ? How much does the resistance change if the diameter is doubled?



[Watch Video Solution](#)

7. The values of current  $I$  flowing in a given resistor for the corresponding values of potential difference  $V$  across the resistor are given below –

$I$ (amperes)	0.5	1.0	2.0	3.0	4.0
$V$ (volts)	1.6	3.4	6.7	10.2	13.2

Plot a graph between  $V$  and  $I$  and calculate the resistance of that resistor.



 [Watch Video Solution](#)

8. When a 12 V battery is connected across an unknown resistor, there is a current of 2.5 mA in the circuit. Find the value of the resistance of the resistor.

 [Watch Video Solution](#)

9. A battery of 9 V is connected in series with resistors of  $0.2\Omega$ ,  $0.3\Omega$ ,  $0.4\Omega$ ,  $0.5\Omega$  and  $12\Omega$ , respectively. How much current would flow through the  $12\Omega$  resistor?

 [Watch Video Solution](#)

**10.** How many  $176 \Omega$  resistors (in parallel) are required to carry 5 A on a 220 V line?

 [Watch Video Solution](#)

**11.** Show how you would connect three resistors, each of resistance  $6 \Omega$ , so that the combination has a resistance of (i)  $9 \Omega$ , (ii)  $4 \Omega$ .

 [Watch Video Solution](#)

**12.** Several electric bulbs designed to be used on a 220 V electric supply line, are rated 10 W. How many lamps can be connected in parallel with each other across the two wires of 220 V line if the maximum allowable current is 5 A?



**Watch Video Solution**

**13.** A hot plate of an electric oven connected to a 220 V line has two resistance coils A and B, each of 24  $\Omega$  resistance, which may be used separately, in series, or in parallel. What are the currents in the three cases?



[Watch Video Solution](#)

**14.** Compare the power used in the  $2\Omega$  resistor in each of the following circuits: (i) a 6 V battery in series with  $1\Omega$  and  $2\Omega$  resistors, and (ii) a 4 V battery in parallel with  $12\Omega$  and  $2\Omega$  resistors.



[Watch Video Solution](#)

**15.** Two lamps, one rated 100 W at 220 V, and the other 60 W at 220 V, are connected in parallel to electric mains supply. What current is drawn from the line if the supply voltage is 220 V?

 [Watch Video Solution](#)

**16.** Which uses more energy, a 250 W TV set in 1 hr, or a 1200 W toaster in 10 minutes?

 [Watch Video Solution](#)

**17.** An electric heater of resistance  $8 \Omega$  draws 15 A from the service mains 2 hours. Calculate the rate at which heat is developed in the heater.

 [Watch Video Solution](#)

**18.** Explain the following.

(a) Why is the tungsten used almost exclusively for filament of electric lamps?

(b) Why are the conductors of electric heating devices, such as bread-toasters and electric irons, made of an alloy rather than a pure metal?

(c) Why is the series arrangement not used for domestic circuits?

(d) How does the resistance of a wire vary with its area of cross-section?

(e) Why are copper and aluminium wires usually employed for electricity transmission?



**Watch Video Solution**

